

Lecture 8

Understanding EM using Resistor-inductor (RL) circuit

GEOL 4397: Electromagnetic Methods for Exploration
GEOL 6398: Special Problems

Jiajia Sun, Ph.D.

Sept. 18th/20th, 2018

UNIVERSITY of
HOUSTON

YOU ARE THE PRIDE


EARTH AND ATMOSPHERIC SCIENCES

Outline

- Inductance
- RL circuit under DC
- RL circuit under AC
- Understanding frequency domain EM using RL circuit
- Understanding time domain EM using RL circuit

Inductance

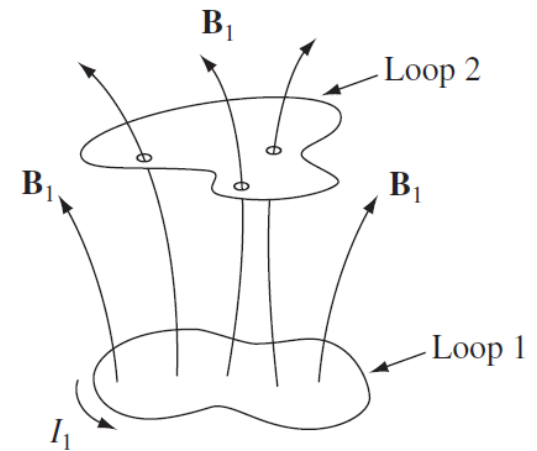- Imagine two loops of wire at rest
- If we run a steady current I_1 around loop 1, it produces a magnetic field \mathbf{B}_1




Griffiths, 4th edition, pp 322

Inductance

- Imagine two loops of wire at rest
- If we run a steady current I_1 around loop 1, it produces a magnetic field \mathbf{B}_1
- According to Biot-Savart law,
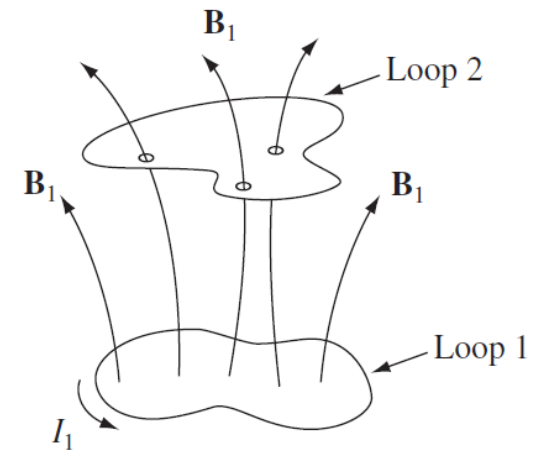
$$\mathbf{B}_1 = \frac{\mu_0}{4\pi} I_1 \oint \frac{d\mathbf{I}'_1 \times \hat{\mathbf{r}}}{r^2}$$




Griffiths, 4th edition, pp 322

Inductance

- Imagine two loops of wire at rest
- If we run a steady current I_1 around loop 1, it produces a magnetic field \mathbf{B}_1
- According to Biot-Savart law,

$$\mathbf{B}_1 = \frac{\mu_0}{4\pi} I_1 \oint \frac{d\mathbf{I}'_1 \times \hat{\mathbf{r}}}{r^2}$$

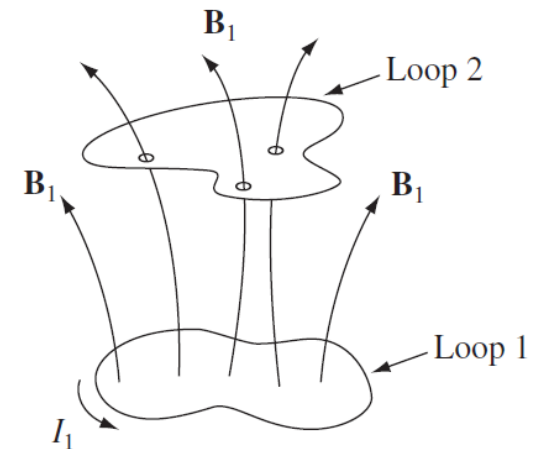- We observe that, the magnetic field is proportional to the current I_1




Griffiths, 4th edition, pp 322

Inductance

- Imagine two loops of wire at rest
- If we run a steady current I_1 around loop 1, it produces a magnetic field \mathbf{B}_1
- According to Biot-Savart law,

$$\mathbf{B}_1 = \frac{\mu_0}{4\pi} I_1 \oint \frac{d\mathbf{I}'_1 \times \hat{\mathbf{r}}}{r^2}$$

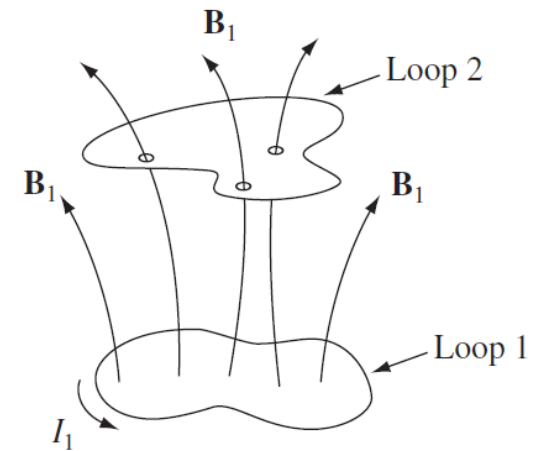- We observe that, the magnetic field is proportional to the current I_1
- Some of the magnetic field lines pass through loop 2



Griffiths, 4th edition, pp 322


Inductance

- Imagine two loops of wire at rest
- If we run a steady current I_1 around loop 1, it produces a magnetic field \mathbf{B}_1
- According to Biot-Savart law,

$$\mathbf{B}_1 = \frac{\mu_0}{4\pi} I_1 \oint \frac{d\mathbf{I}'_1 \times \hat{\mathbf{r}}}{r^2}$$

- We observe that, the magnetic field is proportional to the current I_1
- Some of the magnetic field lines pass through loop 2
- The flux of \mathbf{B}_1 through loop 2 is
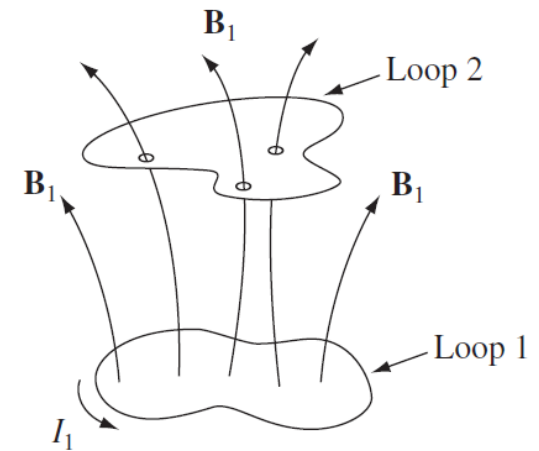
$$\Phi_2 = \int \mathbf{B}_1 \cdot d\mathbf{a}_2$$



Griffiths, 4th edition, pp 322

Inductance


- Imagine two loops of wire at rest
- If we run a steady current I_1 around loop 1, it produces a magnetic field \mathbf{B}_1
- According to Biot-Savart law,

$$\mathbf{B}_1 = \frac{\mu_0}{4\pi} I_1 \oint \frac{d\mathbf{I}'_1 \times \hat{\mathbf{r}}}{r^2}$$

- We observe that, the magnetic field is proportional to the current I_1
- Some of the magnetic field lines pass through loop 2
- The flux of \mathbf{B}_1 through loop 2 is

$$\Phi_2 = \int \mathbf{B}_1 \cdot d\mathbf{a}_2$$

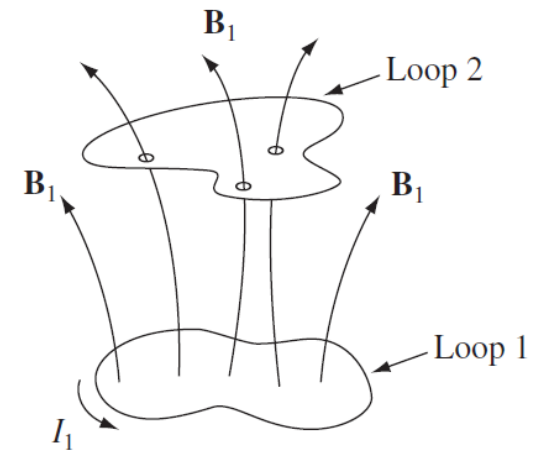which is also proportional to the current I_1



Griffiths, 4th edition, pp 322

Inductance

- Imagine two loops of wire at rest
- If we run a steady current I_1 around loop 1, it produces a magnetic field \mathbf{B}_1
- According to Biot-Savart law,

$$\mathbf{B}_1 = \frac{\mu_0}{4\pi} I_1 \oint \frac{d\mathbf{I}'_1 \times \hat{\mathbf{r}}}{r^2}$$

- We observe that, the magnetic field is proportional to the current I_1
- Some of the magnetic field lines pass through loop 2
- The flux of \mathbf{B}_1 through loop 2 is


$$\Phi_2 = \int \mathbf{B}_1 \cdot d\mathbf{a}_2$$

which is also proportional to the current I_1

- Therefore,

$$\Phi_2 = M_{21} I_1$$

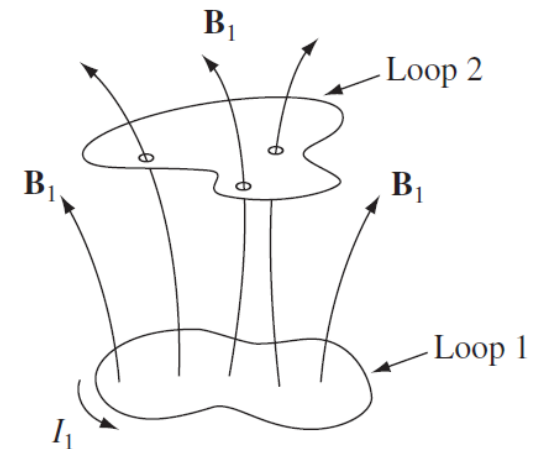where M_{21} is the constant of proportionality known as the **mutual inductance** of the two loops



Griffiths, 4th edition, pp 322

Mutual inductance (optional)

- We derive a formula for M_{21} using vector potential and Stokes' theorem

$$\Phi_2 = \int \mathbf{B}_1 \cdot d\mathbf{a}_2 = \int (\nabla \times \mathbf{A}_1) \cdot d\mathbf{a}_2 = \oint \mathbf{A}_1 \cdot d\mathbf{I}_2$$

- According to eq 5.66 in Griffiths' book (fourth edition)

$$\mathbf{A}_1 = \frac{\mu_0 I_1}{4\pi} \oint \frac{d\mathbf{I}_1}{r}$$

- Therefore,

$$\Phi_2 = \frac{\mu_0 I_1}{4\pi} \oint \left(\oint \frac{d\mathbf{I}_1}{r} \right) \cdot d\mathbf{I}_2$$

- Therefore,

$$M_{21} = \frac{\mu_0}{4\pi} \oint \oint \frac{d\mathbf{I}_1 \cdot d\mathbf{I}_2}{r}$$

Griffiths, 4th edition, pp 322

Mutual inductance

Observations:

- M_{21} is a **purely geometrical** quantity, having to do with the sizes, shapes, and relative positions of the two loops
- $M_{21} = M_{12}$


Whatever the shapes and positions of the loops, the flux through loop 2 due to current I in loop 1 is identical to the flux through loop 1 due to current I in loop 2.

We can then drop the subscripts, and call them both M .

Griffiths, 4th edition, pp 323

EMF

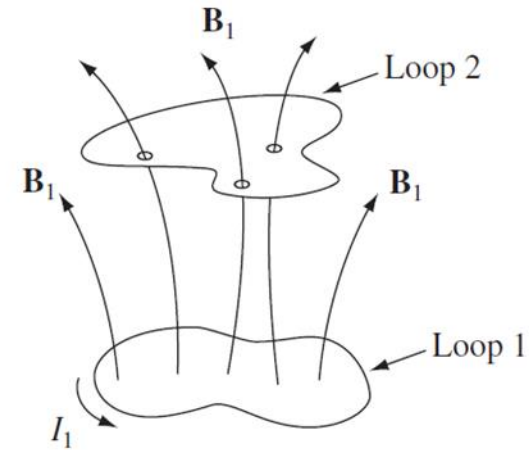- If we vary the current in loop 1, the flux through loop 2 will vary accordingly.




Griffiths, 4th edition, pp 324

EMF

- If we vary the current in loop 1, the flux through loop 2 will vary accordingly.
- According to Faraday's law, the changing flux will induce an emf in loop 2
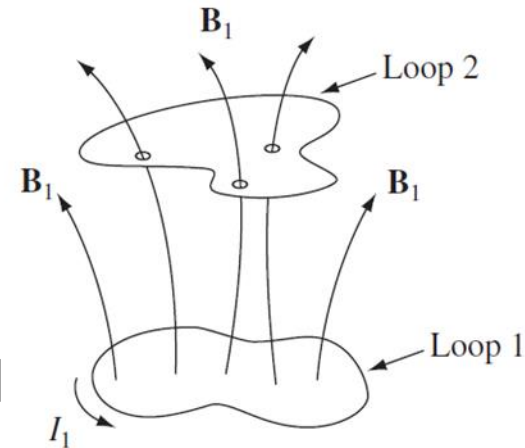
$$\varepsilon_2 = -\frac{d\Phi_2}{dt} = -M \frac{dI_1}{dt}$$




Griffiths, 4th edition, pp 324

EMF

- If we vary the current in loop 1, the flux through loop 2 will vary accordingly.
- According to Faraday's law, the changing flux will induce an emf in loop 2

$$\varepsilon_2 = -\frac{d\Phi_2}{dt} = -M \frac{dI_1}{dt}$$

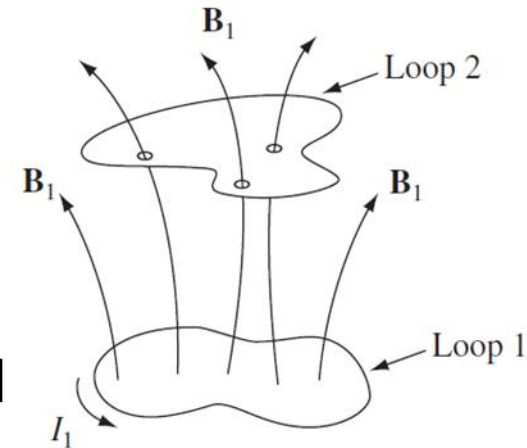- Here we assume that the currents change slowly enough that the system can be considered quasi-static, and Biot-Savart law still holds.
- This is the **EMF** induced in one circuit by a current flowing in another circuit (**amazing!**).



Griffiths, 4th edition, pp 324

Self inductance

- Changing current in loop 1 not only induces an emf in loop 2, but also induces an emf in itself.

Griffiths, 4th edition, pp 324

Self inductance

- Changing current in loop 1 not only induces an emf in loop 2, but also induces an emf in itself.
- The flux through loop 1 is proportional to the current

$$\Phi = LI$$

Griffiths, 4th edition, pp 324

Self inductance

- Changing current in loop 1 not only induces an emf in loop 2, but also induces an emf in itself.
- The flux through loop 1 is proportional to the current

$$\Phi = LI$$

- L : self inductance (or simply inductance)

Griffiths, 4th edition, pp 324

Self inductance

- Changing current in loop 1 not only induces an emf in loop 2, but also induces an emf in itself.
- The flux through loop 1 is proportional to the current

$$\Phi = LI$$

- L : self inductance (or simply inductance)
- Only depends on the geometry (size and shape) of the loop.

Griffiths, 4th edition, pp 324

Self inductance

- Changing current in loop 1 not only induces an emf in loop 2, but also induces an emf in itself.
- The flux through loop 1 is proportional to the current

$$\Phi = LI$$

- L : **self inductance** (or simply **inductance**)
- Only depends on the **geometry (size and shape) of the loop**.
- If the current changes, the emf induced in the loop is

$$\varepsilon = -L \frac{dI}{dt}$$

Griffiths, 4th edition, pp 324

Back EMF

- The **minus sign** in the previous equation reflects **Lenz's law**, which says that the emf is in such a direction as to **oppose any change** in current.

Griffiths, 4th edition, pp 325

Back EMF

- The **minus sign** in the previous equation reflects **Lenz's law**, which says that the emf is in such a direction as to **oppose any change** in current.
- Therefore, it is also called **back emf**.

Griffiths, 4th edition, pp 325

Back EMF

- The **minus sign** in the previous equation reflects **Lenz's law**, which says that the emf is in such a direction as to **oppose any change** in current.
- Therefore, it is also called **back emf**.
- Whenever you try to alter the current in a wire, you must fight against this back emf.

Griffiths, 4th edition, pp 325

Back EMF

- The minus sign in the previous equation reflects Lenz's law, which says that the emf is in such a direction as to oppose any change in current.
- Therefore, it is also called back emf.
- Whenever you try to alter the current in a wire, you must fight against this back emf.
- **Inductance** plays somewhat the same role in **electric circuits** that **mass** plays in **mechanical system**: The greater L is, the harder it is to change the current, just as the larger the mass, the harder it is to change an object's velocity.


Griffiths, 4th edition, pp 325

Outline

- Inductance
- RL circuit under DC
- RL circuit under AC
- Understanding frequency domain EM using RL circuit
- Understanding time domain EM using RL circuit

Kirchhoff's voltage law (KVL)

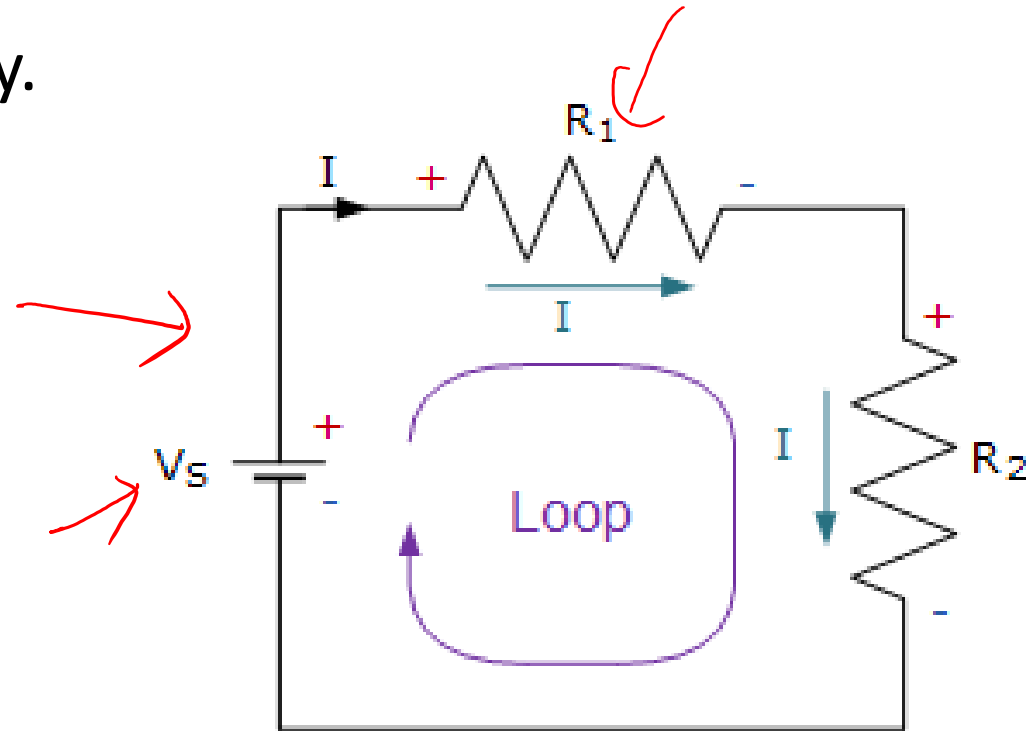
- The algebraic sum of all the **voltages** (or, **potential differences**) around any close loop in a circuit is 0.
- Conservation of energy.



<https://www.electronics-tutorials.ws/dccircuits/kirchhoffs-voltage-law.html>

Kirchhoff's voltage law (KVL)

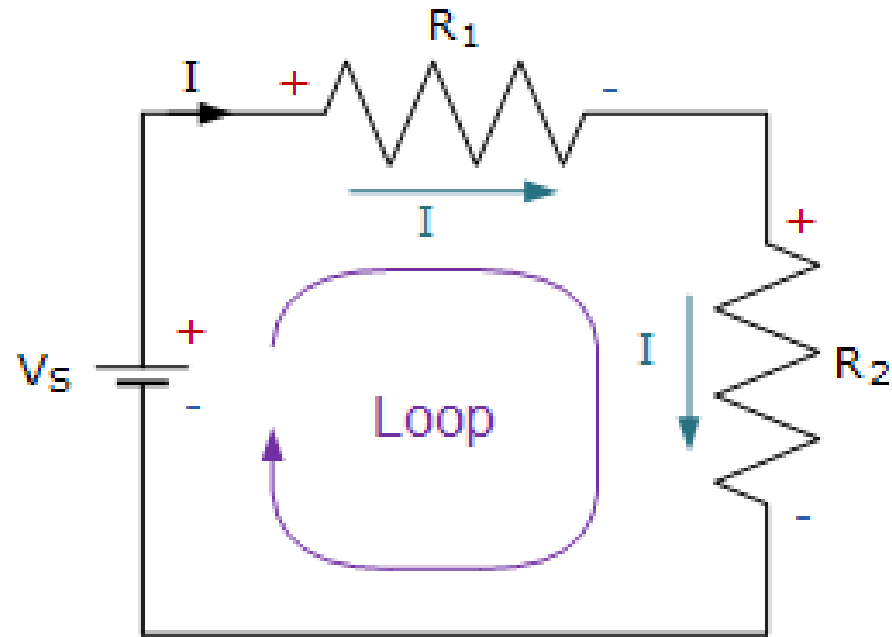- The algebraic sum of all the **voltages** (or, **potential differences**) around any close loop in a circuit is 0.
- Conservation of energy.
- Current must be the same because of series connection
- The voltage drop across $R_1 : IR_1$
- The voltage drop across $R_2 : IR_2$
- Suppose the voltage from the battery is V_s
- Then,
$$V_s - IR_1 - IR_2 = 0$$




<https://www.electronics-tutorials.ws/dccircuits/kirchhoffs-voltage-law.html>


DC RL circuit

L: inductor

R: resistor

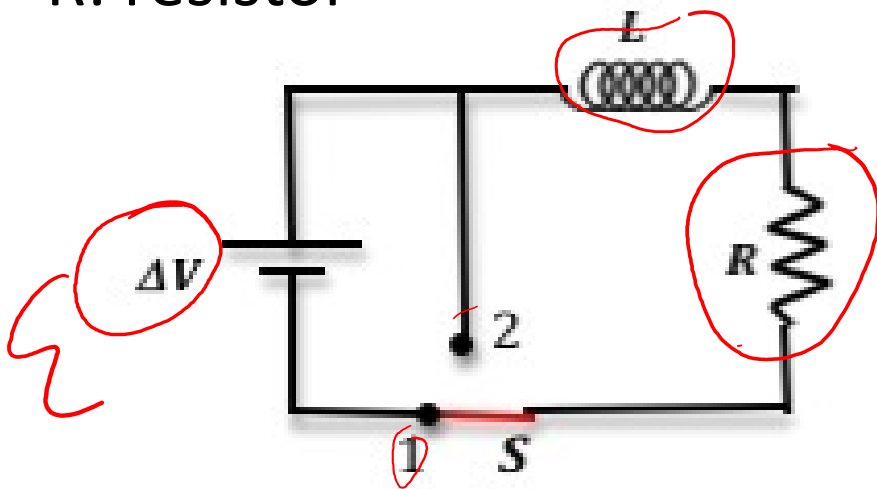

(a)

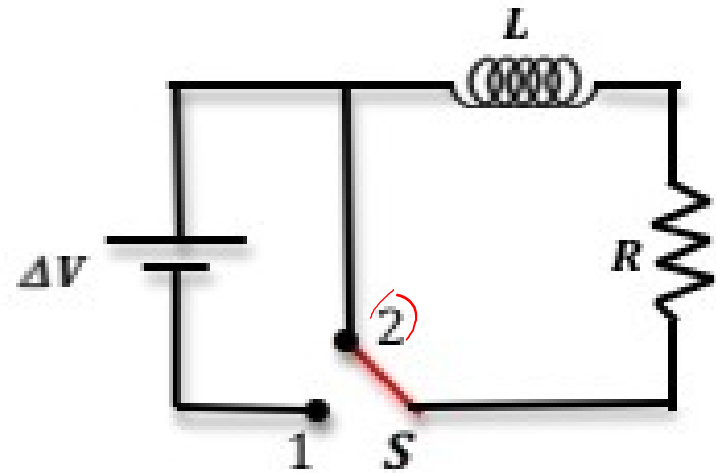


(b)

Inductance: the tendency of a circuit to oppose any changes in the current (or magnetic flux).

http://www.webassign.net/labsgraceperiod/ncsulcpem2/lab_7/manual.html


DC RL circuit: energizing

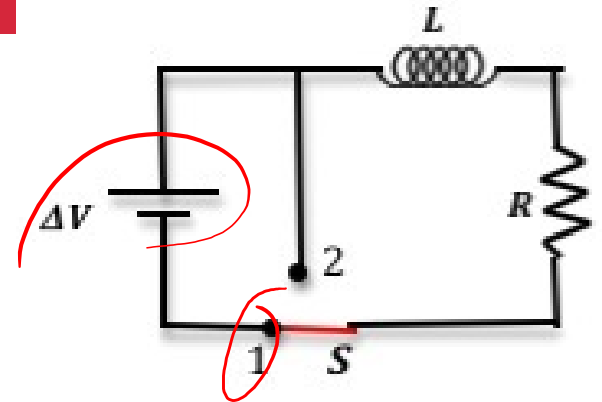

- From a physical point of view, what physical phenomena would happen if the switch is closed?

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html


DC RL circuit: energizing

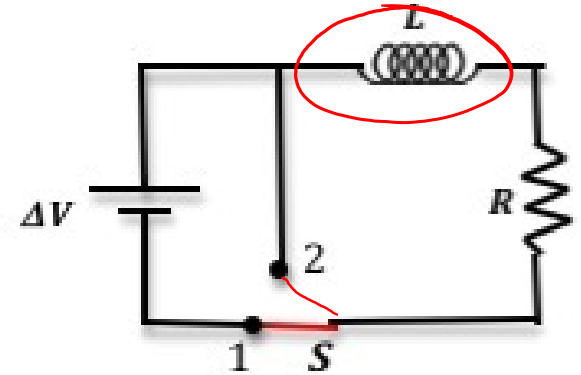

- From a physical point of view, what physical phenomena would happen if the switch is closed?
- Current will flow.

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html


DC RL circuit: energizing

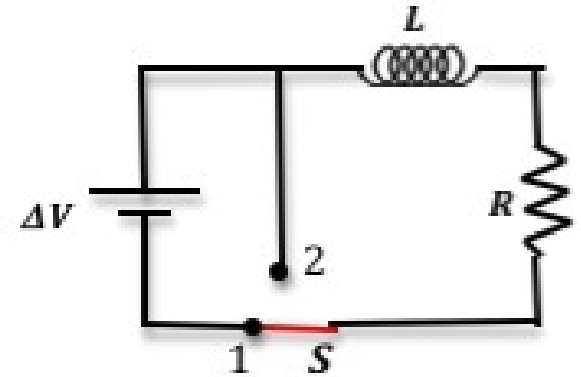

- From a physical point of view, what physical phenomena would happen if the switch is closed?
- Current will flow.
- A back emf will occur across the inductor!

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: energizing

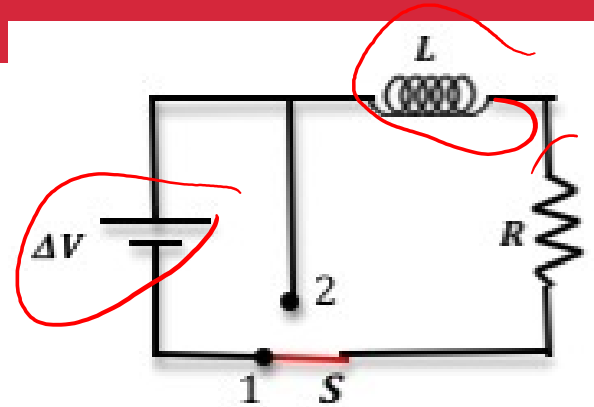


- From a physical point of view, what physical phenomena would happen if the switch is closed?
- Current will flow.
- A back emf will occur across the inductor!
- Now, let us write out the Kirchhoff's loop equation.

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: energizing

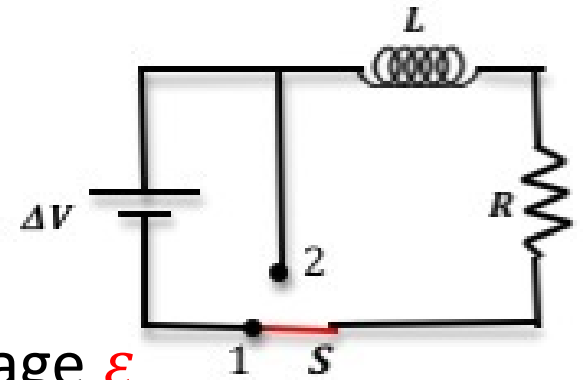
- R and L are connected in series with voltage \mathcal{E}



Griffiths, 4th edition, pp 326

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: energizing

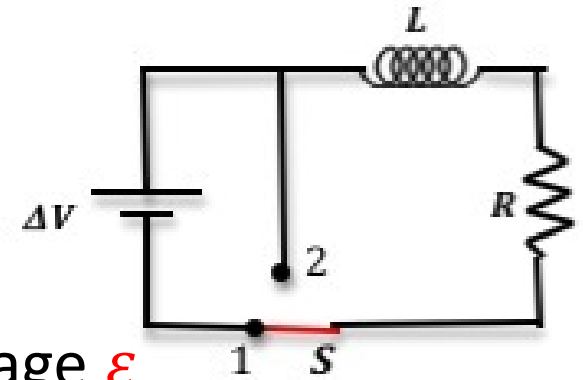


- R and L are connected in series with voltage \mathcal{E}
- Therefore, the same current I flowing in the circuit

Griffiths, 4th edition, pp 326

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: energizing

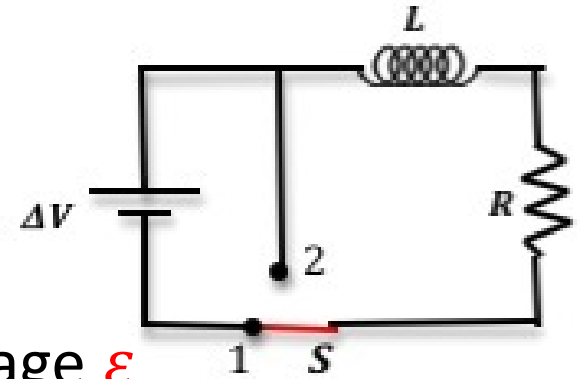


- R and L are connected in series with voltage ε
- Therefore, the same current I flowing in the circuit
- The total emf in the circuit is ε from the battery plus $-L\left(\frac{dI}{dt}\right)$ from the inductance. Ohm's law says

Griffiths, 4th edition, pp 326

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: energizing

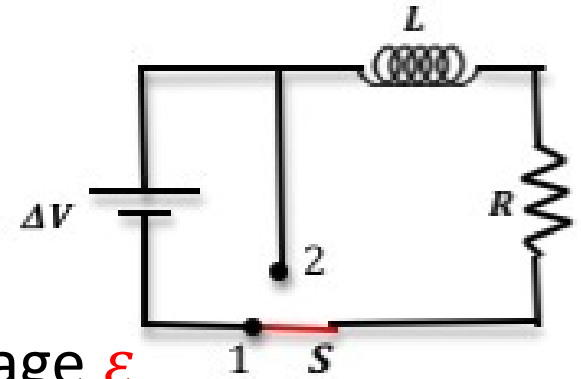


- R and L are connected in series with voltage ε
- Therefore, the same current I flowing in the circuit
- The total emf in the circuit is ε from the battery plus $-L\left(\frac{dI}{dt}\right)$ from the inductance. Ohm's law says

$$\varepsilon - L \frac{dI}{dt} = IR$$

Griffiths, 4th edition, pp 326

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: energizing

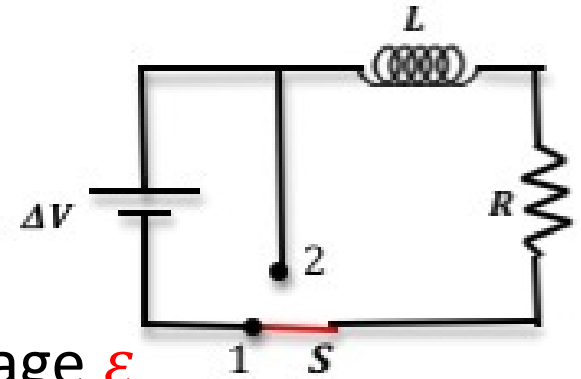

- R and L are connected in series with voltage ε
- Therefore, the same current I flowing in the circuit
- The total emf in the circuit is ε from the battery plus $-L(\frac{dI}{dt})$ from the inductance. Ohm's law says

$$\varepsilon - L \frac{dI}{dt} = IR$$

- Solving the above differential equation, we obtain

$$I(t) = \frac{\varepsilon}{R} [1 - e^{-t/\tau}]$$

where $\tau = \frac{L}{R}$ known as **time constant**

Griffiths, 4th edition, pp 326

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

In-class exercise

- Verify the solution

$$I(t) = \frac{\varepsilon}{R} [1 - e^{-t/\tau}], \text{ where } \tau = \frac{L}{R}$$



to the differential equation

$$\varepsilon - L \frac{dI}{dt} = IR$$

DC RL circuit: energizing

$$I(t) = \frac{\varepsilon}{R} [1 - e^{-t/\tau}]$$

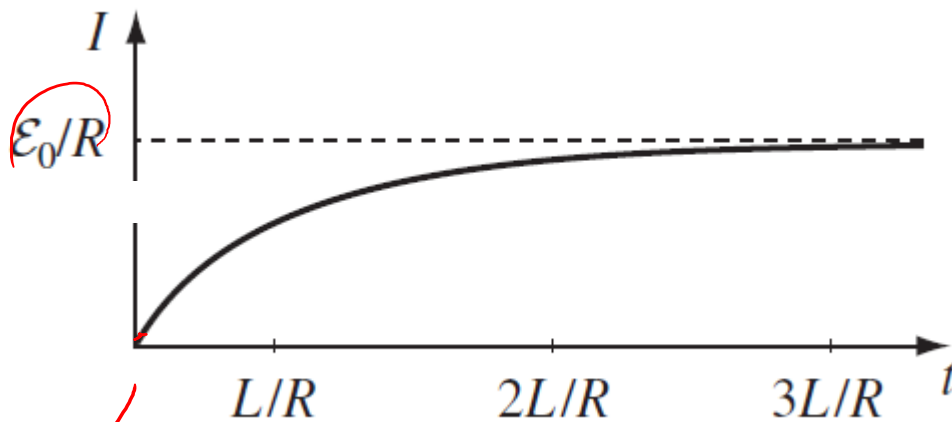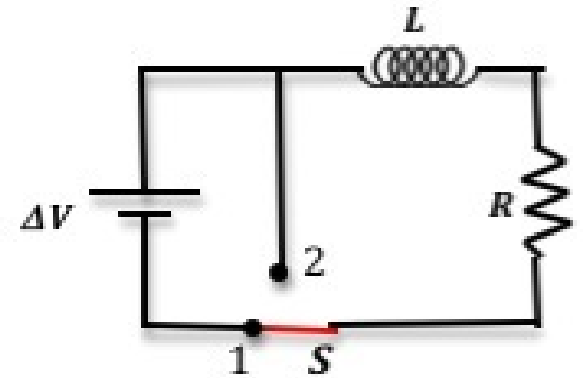where $\tau = \frac{L}{R}$ known as **time constant**





Griffiths, 4th edition, pp 326

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: energizing

$$I(t) = \frac{\varepsilon}{R} [1 - e^{-t/\tau}]$$

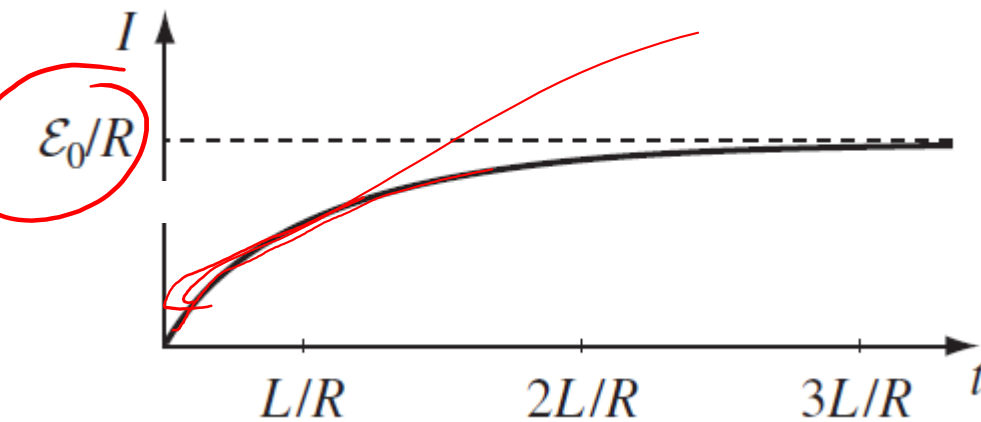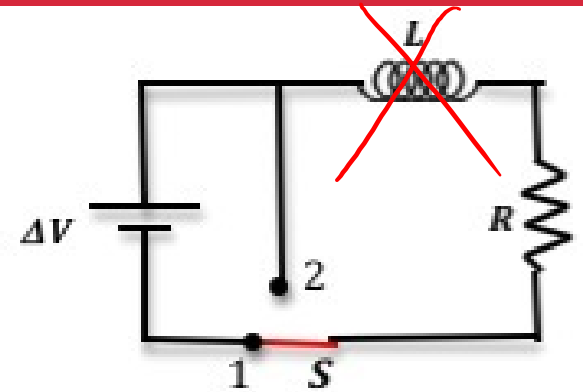where $\tau = \frac{L}{R}$ known as **time constant**




- Had there been no inductance in the circuit, the current would have jumped immediately to ε/R
- In practice, every circuit has some self-inductance
- Time constant tells you how long it takes for the current to reach a substantial fraction (roughly two thirds) of its final value.

Griffiths, 4th edition, pp 326

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html


DC RL circuit: de-energizing

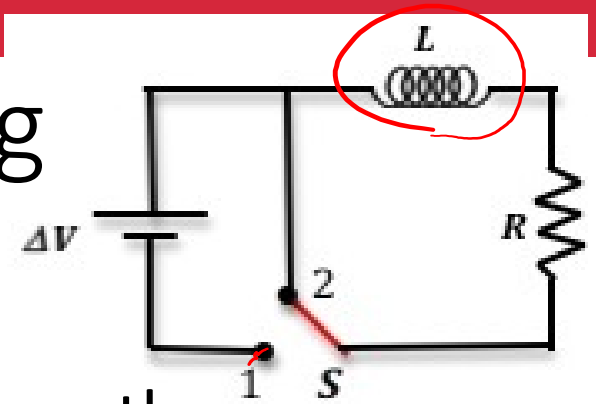

- The total emf in the circuit is $-L\left(\frac{dI}{dt}\right)$ from the inductance. Applying Ohm's law,

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: de-energizing

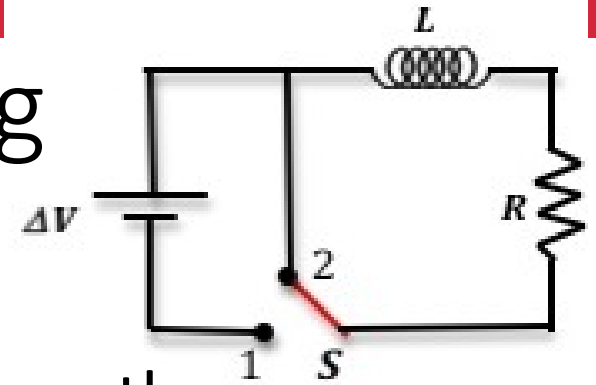


- The total emf in the circuit is $-L\left(\frac{dI}{dt}\right)$ from the inductance. Applying Ohm's law,

$$-L \frac{dI}{dt} = IR$$

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

DC RL circuit: de-energizing

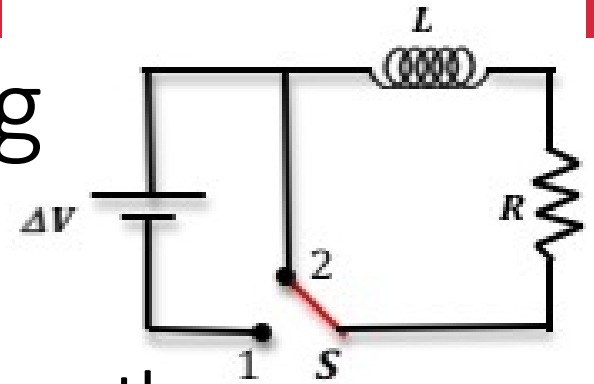

- The total emf in the circuit is $-L\left(\frac{dI}{dt}\right)$ from the inductance. Applying Ohm's law,

$$-L \frac{dI}{dt} = IR$$

- Solving the above differential equation, we obtain

$$I(t) = \frac{\varepsilon}{R} e^{-t/\tau}$$

where $\tau = \frac{L}{R}$ known as time constant

http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html


In-class exercise

- Verify the solution

$$I(t) = \frac{\varepsilon}{R} e^{-t/\tau}, \text{ where } \tau = \frac{L}{R}$$

to the differential equation

$$-L \frac{dI}{dt} = IR$$

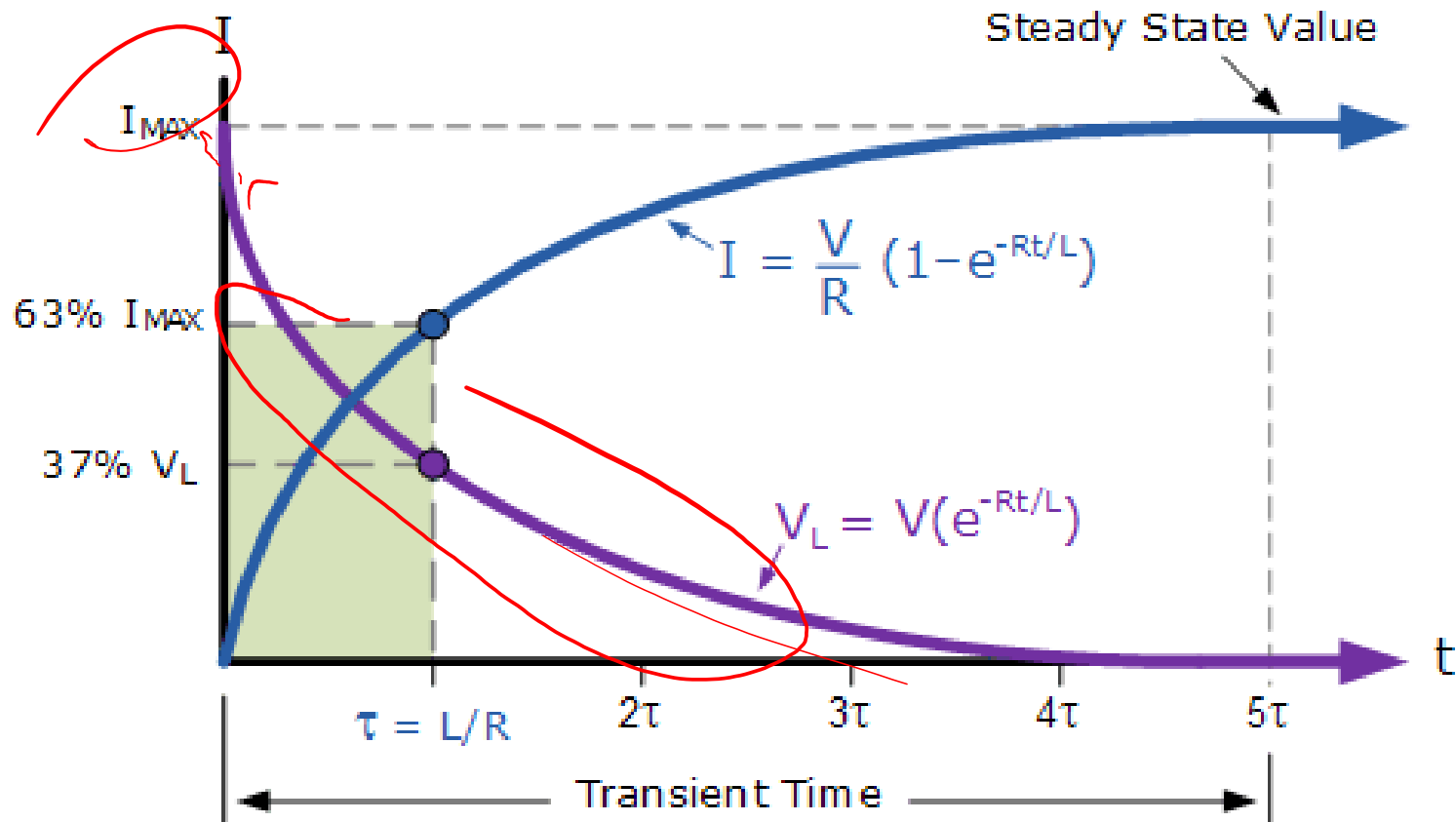


http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html

Resources

- <https://physics.info/circuits-rl/>
- http://www.physics.louisville.edu/cldavis/phys299/notes/mag_LR.html
- http://www.webassign.net/labsgraceperiod/ncsulcpem2/lab_7/manual.html
- <https://www.electrical4u.com/rl-series-circuit/>
- <http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>
- <https://www.york.cuny.edu/academics/departments/earth-and-physical-sciences/physics-lab-manuals/physics-ii/alternating-current-rl-circuits>

AC RL circuit

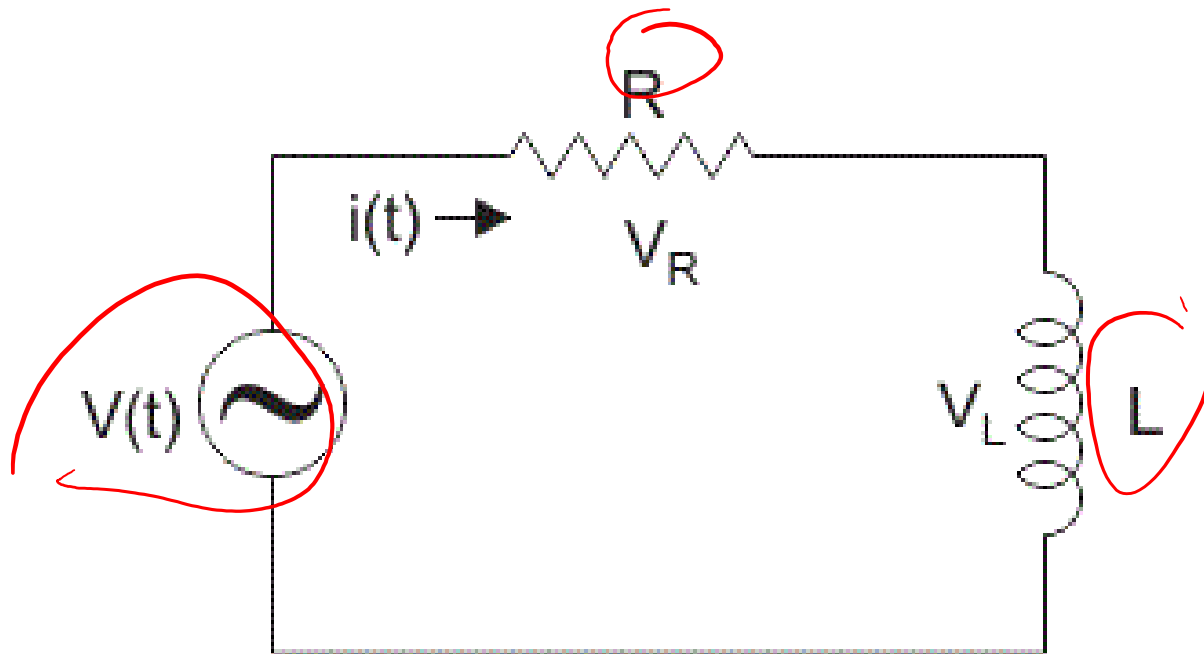


<https://www.electrical4u.com/rl-series-circuit/>

Simple AC circuits


Purely resistive load

A purely resistive circuit corresponds to infinite capacitance $C = \infty$ and zero inductance $L = 0$

Applying Kirchhoff's loop rule yields

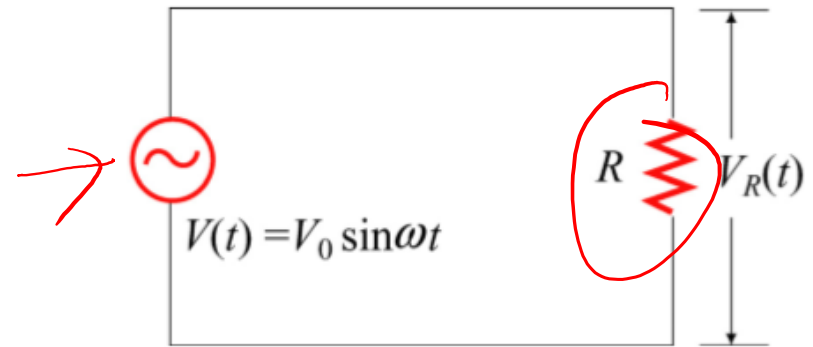
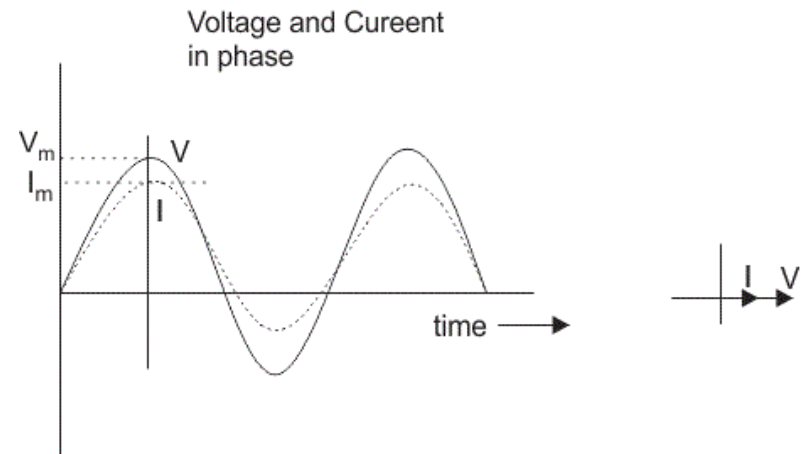
<http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>




<https://www.electrical4u.com/rl-series-circuit/>

Purely resistive load


A purely resistive circuit corresponds to infinite capacitance $C = \infty$ and zero inductance $L = 0$

Applying Kirchhoff's loop rule yields
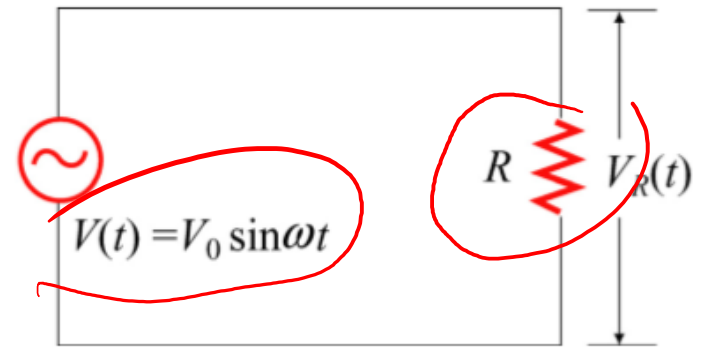
$$\underline{V(t)} = V_R(t) = \underline{I_R(t)} R$$


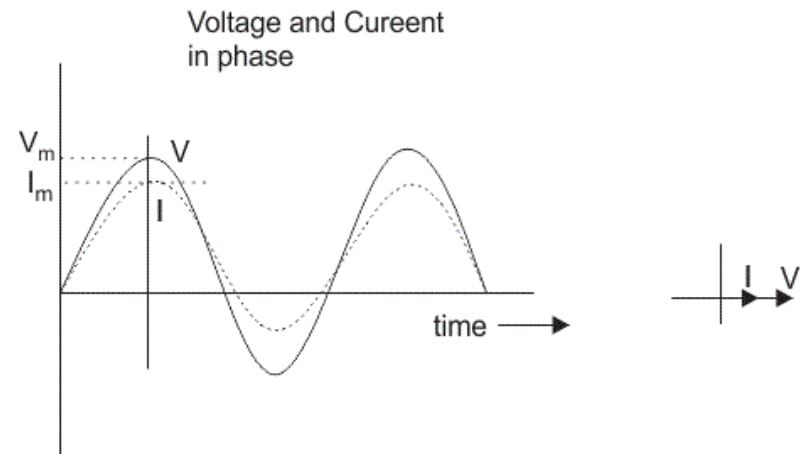
<http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>



<https://www.electrical4u.com/rl-series-circuit/>

Purely resistive load

A purely resistive circuit corresponds to infinite capacitance $C = \infty$ and zero inductance $L = 0$


Applying Kirchhoff's loop rule yields

$$V(t) = V_R(t) = I_R(t)R$$


The current is then

$$I_R(t) = \frac{V_R(t)}{R} = \frac{V_0 \sin(\omega t)}{R} = I_0 \sin(\omega t)$$

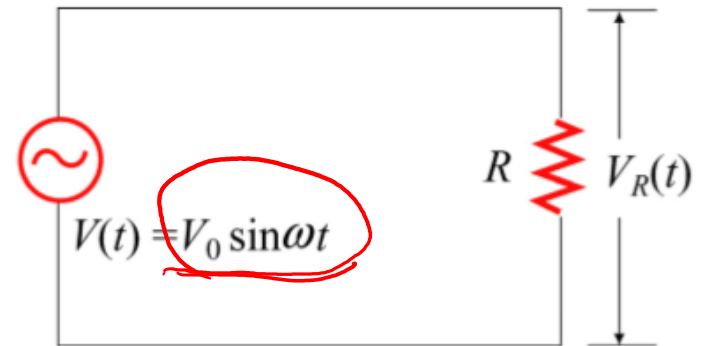In this case, $I_R(t)$ and $V_R(t)$ are **in phase with** each other, meaning that they reach their maximum or minimum values at the same time.


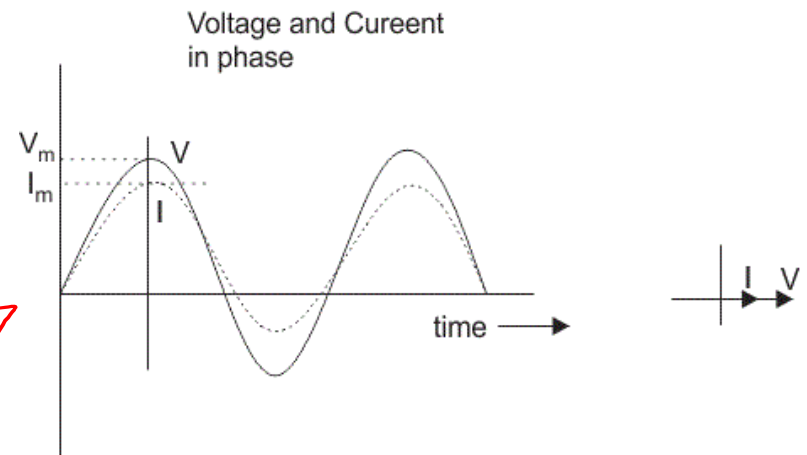
<http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>




<https://www.electrical4u.com/rl-series-circuit/>


Purely inductive load

A purely resistive circuit corresponds to infinite capacitance $C = \infty$ and zero resistance $R = 0$

Applying Kirchhoff's loop rule yields

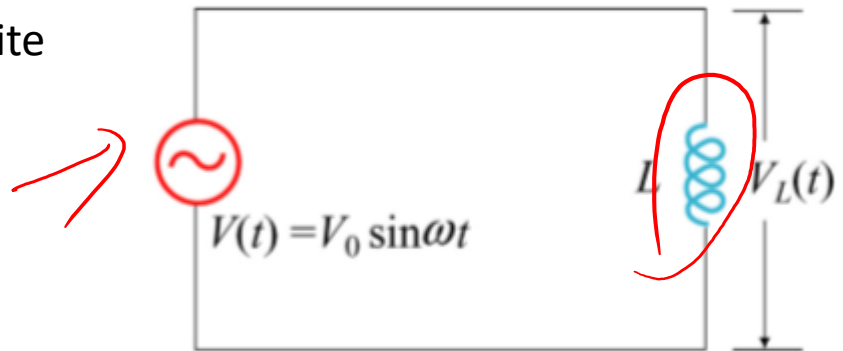
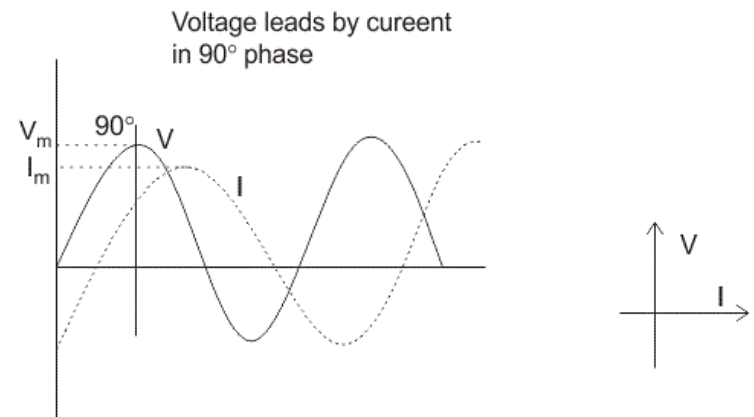
<http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>




<https://www.electrical4u.com/rl-series-circuit/>

Purely inductive load


A purely resistive circuit corresponds to infinite capacitance $C = \infty$ and zero resistance $R = 0$

Applying Kirchhoff's loop rule yields

$$V(t) - L \frac{dI_L}{dt} = 0$$

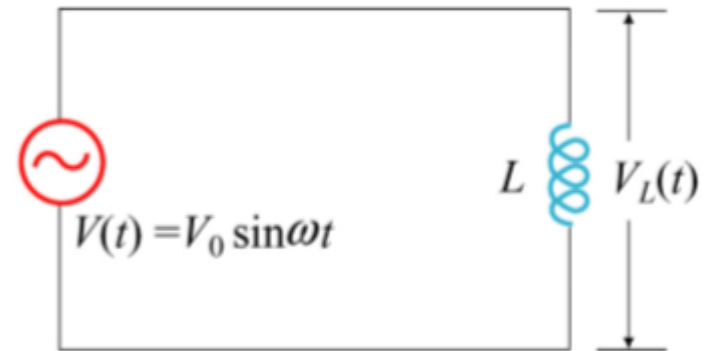
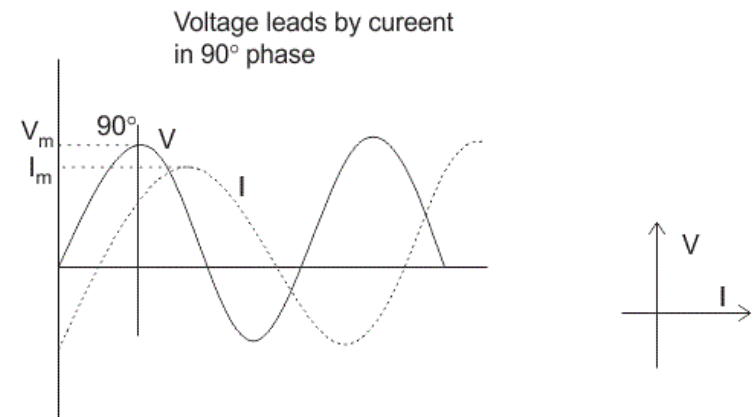
<http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>



<https://www.electrical4u.com/rl-series-circuit/>

Purely inductive load

A purely resistive circuit corresponds to infinite capacitance $C = \infty$ and zero resistance $R = 0$

Applying Kirchhoff's loop rule yields


$$V(t) - L \frac{dI_L}{dt} = 0$$

Then, $\frac{dI_L}{dt} = \frac{V(t)}{L} = \frac{V_0 \sin(\omega t)}{L}$


$I_L(t)$

$$= \int dI_L = \frac{V_0}{L} \int \sin(\omega t) dt = -\left(\frac{V_0}{\omega L}\right) \cos(\omega t) = \left(\frac{V_0}{\omega L}\right) \sin\left(\omega t - \frac{\pi}{2}\right)$$

Voltage leads by current in 90° phase

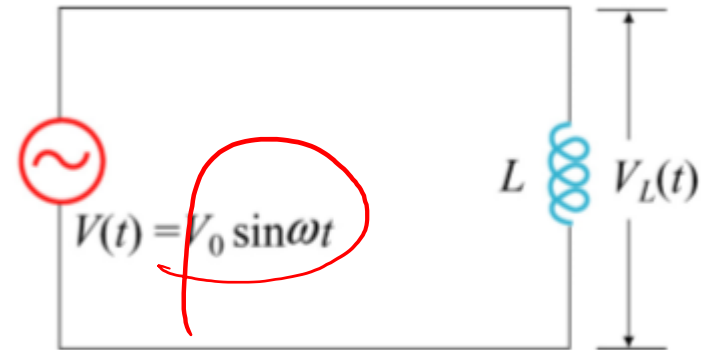
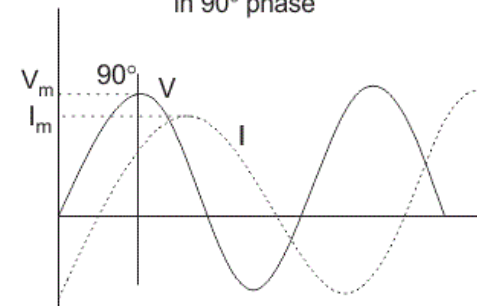
<http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>



<https://www.electrical4u.com/rl-series-circuit/>

Purely inductive load

A purely resistive circuit corresponds to infinite capacitance $C = \infty$ and zero resistance $R = 0$

Applying Kirchhoff's loop rule yields


$$V(t) - L \frac{dI_L}{dt} = 0$$

Then, $\frac{dI_L}{dt} = \frac{V(t)}{L} = \frac{V_0 \sin(\omega t)}{L}$
 $I_L(t)$


$$\int dI_L = \frac{V_0}{L} \int \sin(\omega t) dt = -\left(\frac{V_0}{\omega L}\right) \cos(\omega t) = \left(\frac{V_0}{\omega L}\right) \sin\left(\omega t - \frac{\pi}{2}\right)$$

In this case, the current $I_L(t)$ is **out of phase** with $V_L(t)$ by $\frac{\pi}{2}$; it reaches its maximum after $V_L(t)$ by one quarter of a cycle.

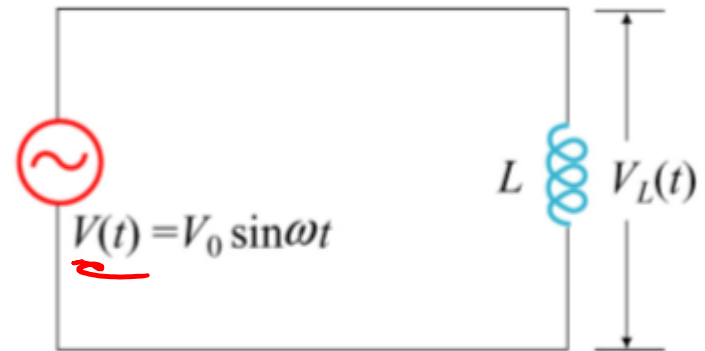The current lags voltage by $\frac{\pi}{2}$ in a purely inductive circuit.


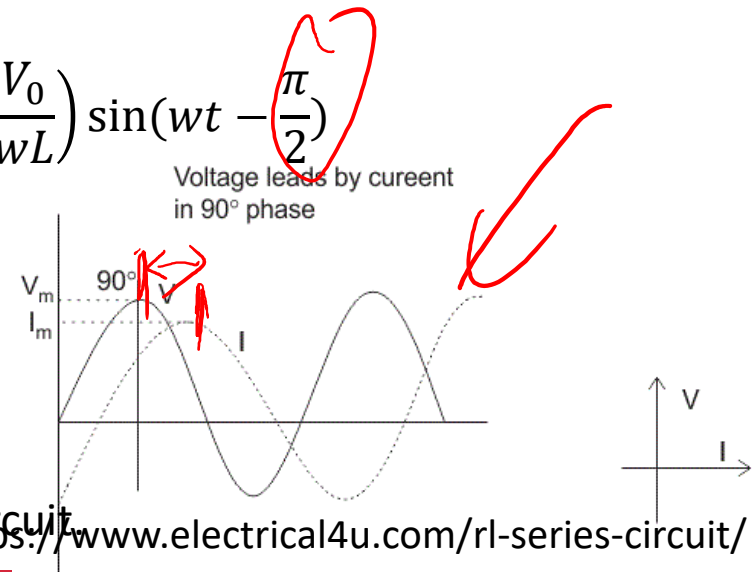
<http://web.mit.edu/viz/EM/visualizations/coursenotes/modules/guide12.pdf>





<https://www.electrical4u.com/rl-series-circuit/>

RL circuits under AC

AC RL circuit

Apply Ohm's law

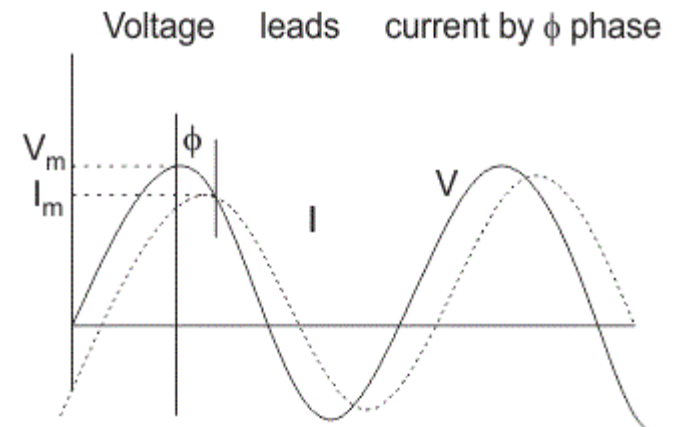
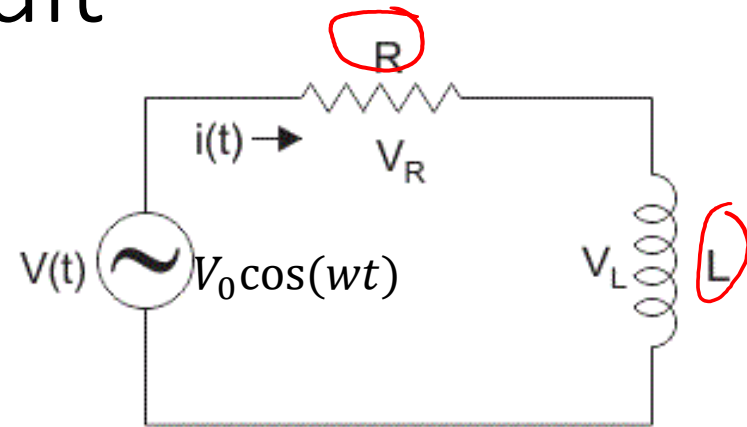


<https://www.electrical4u.com/rl-series-circuit/>

AC RL circuit

Apply Ohm's law
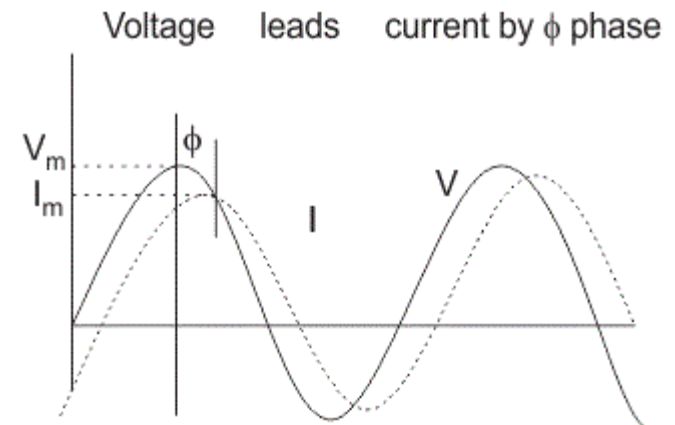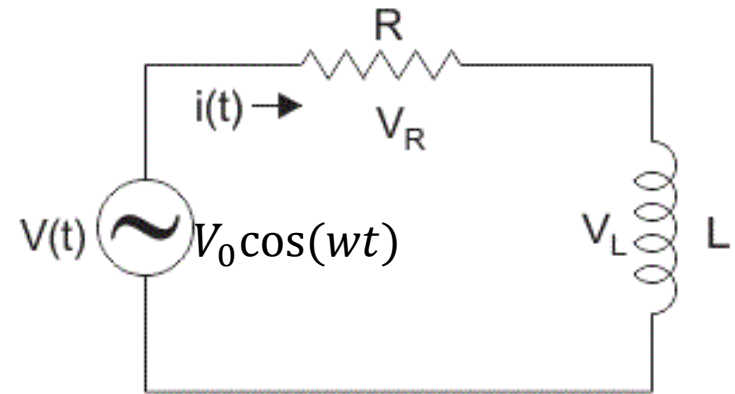
$$V_0 \cos(\omega t) - L \frac{dI(t)}{dt} = I(t)R$$



<https://www.electrical4u.com/rl-series-circuit/>

AC RL circuit

Apply Ohm's law

$$V_0 \cos(\omega t) - L \frac{dI(t)}{dt} = I(t)R$$

Now we need to solve this differential equation

The current $I(t)$ should have the following form:

$$I(t) = I_0 \cos(\omega t - \phi)$$

Substitute into the above differential equation

$$V_0 \cos(\omega t) = -\omega L I_0 \sin(\omega t - \phi) + R I_0 \cos(\omega t - \phi)$$

The right hand side is equal to (<https://goo.gl/hCYkUv>)



$$I_0 \sqrt{R^2 + \omega^2 L^2} \cos(\omega t - \phi - \theta)$$

where $\theta = \tan^{-1}\left(-\frac{\omega L}{R}\right)$

Comparing it with the left hand side term, we obtain

$$I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \text{ and } \phi = -\theta = -\tan^{-1}\left(-\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{\omega L}{R}\right)$$
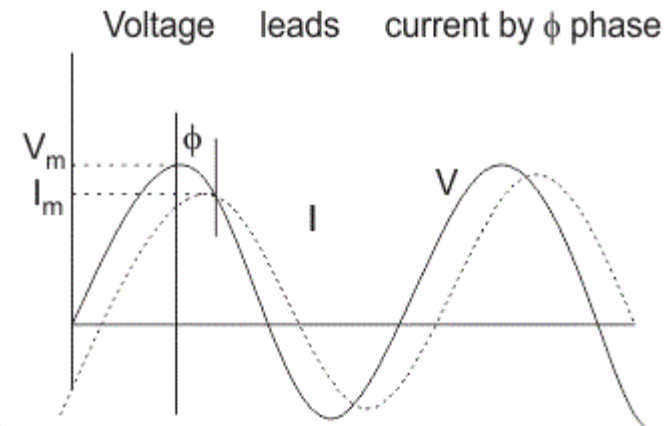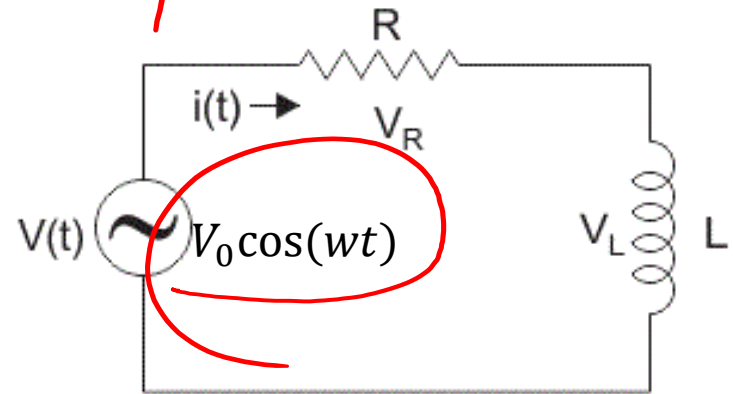
<https://www.electrical4u.com/rl-series-circuit/>



A different derivation (optional) Compare with Ohm's law $I = \frac{V}{R}$, The denominator looks like some measure of electrical impedance

- Previously we obtained that $I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}}$
- Use complex number, the electrical impedance of a RL circuit can be written as

$$Z(\omega) = R + i\omega L$$

Another way of understanding this is to consider the LR circuit in time

- Assume the AC voltage is $V_0 e^{i\omega t}$
- Then the current is simply

$$I = \frac{V_0 e^{i\omega t}}{R + i\omega L}$$

domain $V(t) = I(t)R + L \frac{\partial I(t)}{\partial t}$. In frequency domain, assuming current $I = I_0 e^{i\omega t}$, we have $V = IR + i\omega LI = I(R + i\omega L)$

- How does it compare with what we obtained previously?

$$I = \frac{V_0 e^{i\omega t}}{R + i\omega L} = \frac{V_0 (R - i\omega L) e^{i\omega t}}{R^2 + \omega^2 L^2}$$

$$= \left(\frac{V_0 R}{R^2 + \omega^2 L^2} - i \frac{V_0 \omega L}{R^2 + \omega^2 L^2} \right) e^{i\omega t} = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} e^{i\phi} e^{i\omega t}$$

$$\text{where } \phi = \tan^{-1}\left(-\frac{\omega L}{R}\right)$$

AC RL circuit: conclusions

- In case of **pure resistive** circuit, the phase angle between voltage and current is **zero**
- In case of **pure inductive** circuit, phase angle is **90°**

<https://www.electrical4u.com/rl-series-circuit/>

AC RL circuit: conclusions

- In case of **pure resistive** circuit, the phase angle between voltage and current is **zero**
- In case of **pure inductive** circuit, phase angle is **90°**
- When a circuit has **both a resistor and an inductor**, the phase angle is **between 0° to 90°** .

<https://www.electrical4u.com/rl-series-circuit/>

AC RL circuit: conclusions

- In case of **pure resistive** circuit, the phase angle between voltage and current is **zero**
- In case of **pure inductive** circuit, phase angle is **90°**
- When a circuit has **both a resistor and an inductor**, the phase angle is **between 0° to 90°** .
- If $R \gg L$, e.g., **a strong resistor**, the phase lag is **0**
- If $R \ll L$, e.g., **a perfect conductor**, the phase lag is **90°**

<https://www.electrical4u.com/rl-series-circuit/>

Lecture 9

Understanding EM using Resistor-inductor (RL) circuit

GEOL 4397: Electromagnetic Methods for Exploration
GEOL 6398: Special Problems

Jiajia Sun, Ph.D.

Sept. 20th, 2018

UNIVERSITY of
HOUSTON

YOU ARE THE PRIDE

EARTH AND ATMOSPHERIC SCIENCES


Outline

- Inductance
- RL circuit under DC
- RL circuit under AC
- Understanding frequency domain EM using RL circuit
- Understanding time domain EM using RL circuit

Recap: RL circuit under AC

Kirchhoff equation:
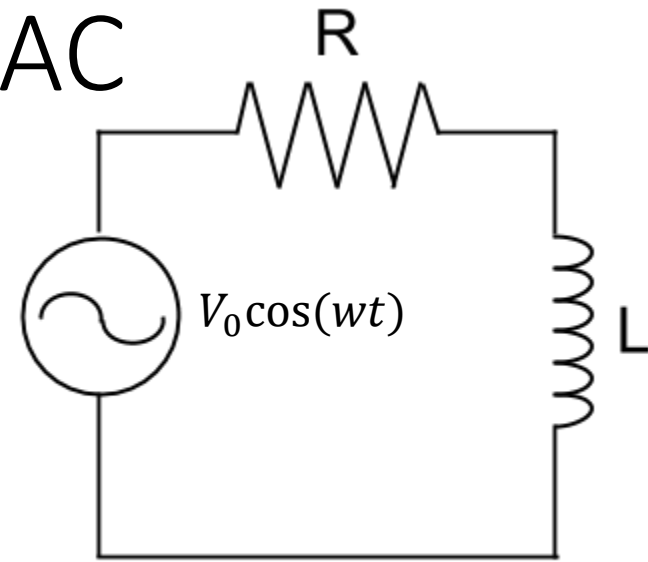
$$V(t) = I(t)R + L \frac{\partial I(t)}{\partial t}$$



Recap: RL circuit under AC

Kirchhoff equation:


$$V(t) = I(t)R + L \frac{\partial I(t)}{\partial t}$$

We can solve the above equation (with some initial condition) to get the current:

$$I(t) = I_0 \cos(\omega t - \phi)$$

where
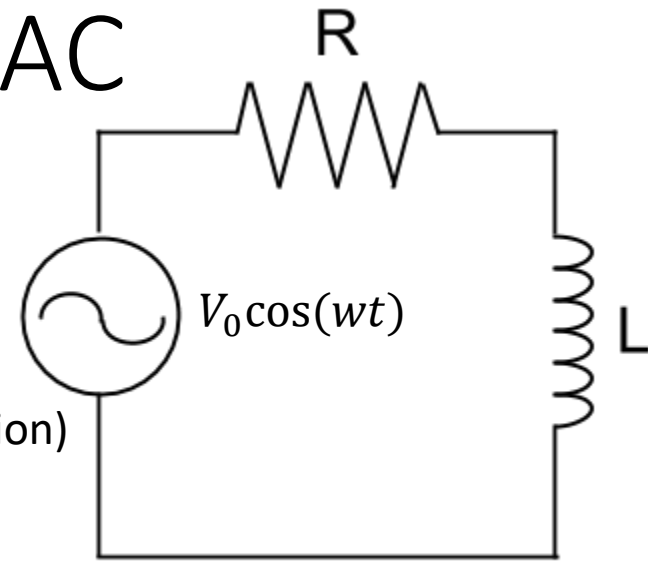
$$I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \text{ and } \phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$



Recap: RL circuit under AC

Kirchhoff equation:

$$V(t) = I(t)R + L \frac{\partial I(t)}{\partial t}$$


We can solve the above equation (with some initial condition) to get the current:

Magnitude **Phase**

$$I(t) = I_0 \cos(\omega t - \phi)$$

where
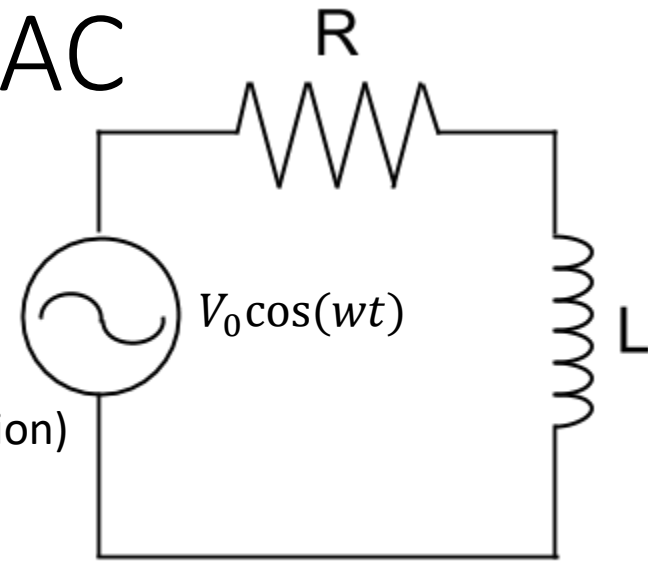
$$I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \text{ and } \phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$



Recap: RL circuit under AC

Kirchhoff equation:

$$V(t) = I(t)R + L \frac{\partial I(t)}{\partial t}$$

We can solve the above equation (with some initial condition) to get the current:

Magnitude **Phase**

$$I(t) = I_0 \cos(\omega t - \phi)$$


where

$$I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \text{ and } \phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$


Another convenient way of expressing current is:

$$I(t) = I_0 e^{i(\omega t - \phi)}$$

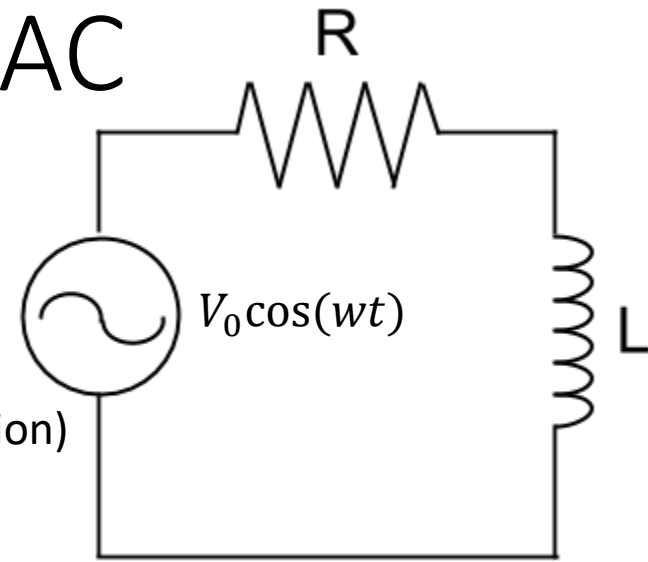
The current lags behind voltage by ϕ in a RL circuit under AC.



Time-domain vs. Frequency domain EM

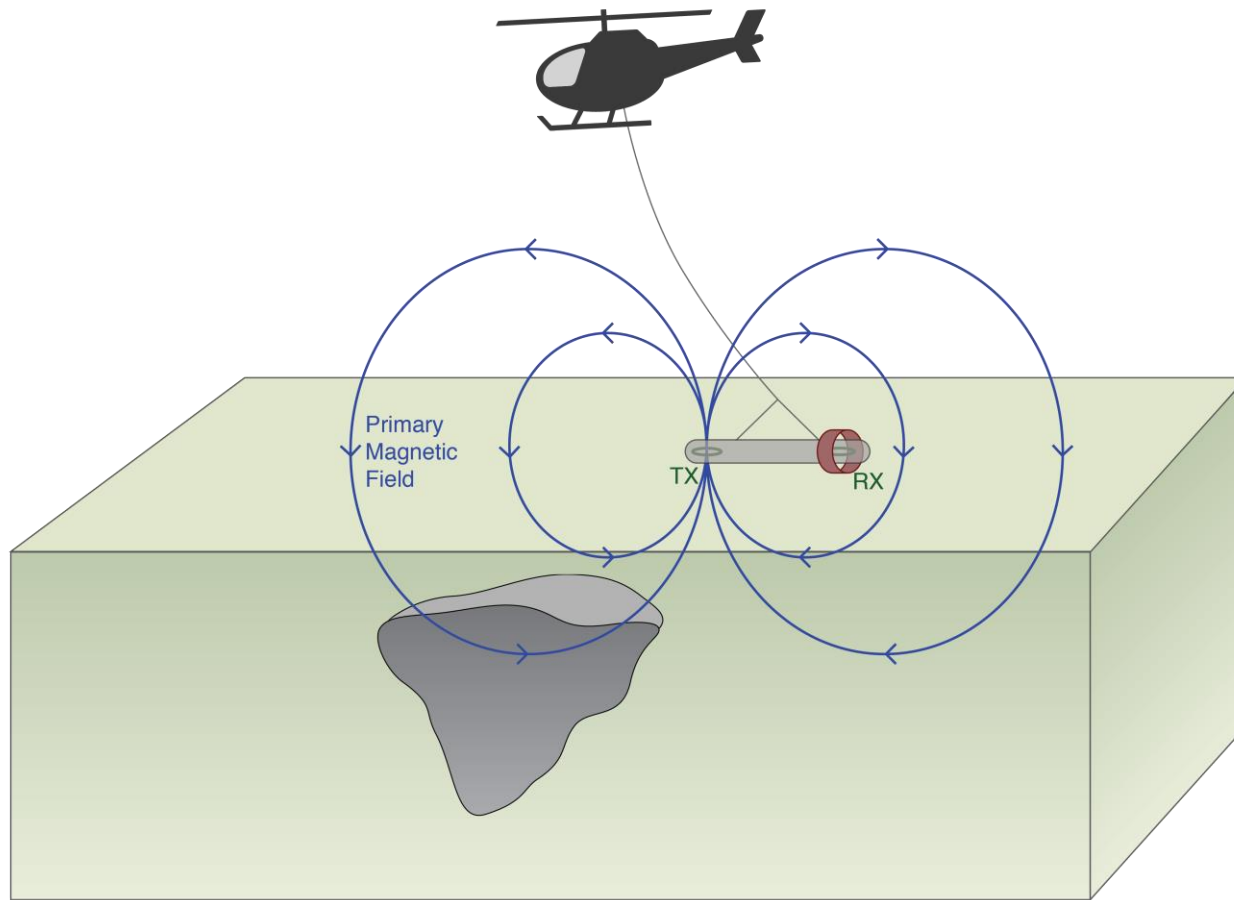

waveform

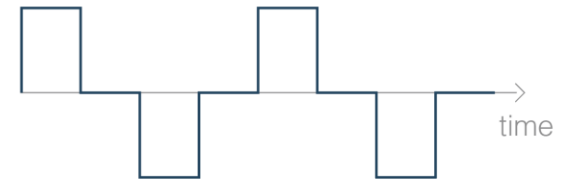

or


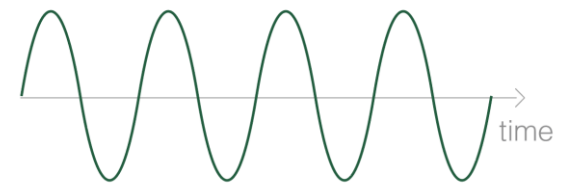


Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF


Airborne EM systems

Area = 535 m²


Resolve system (2008)

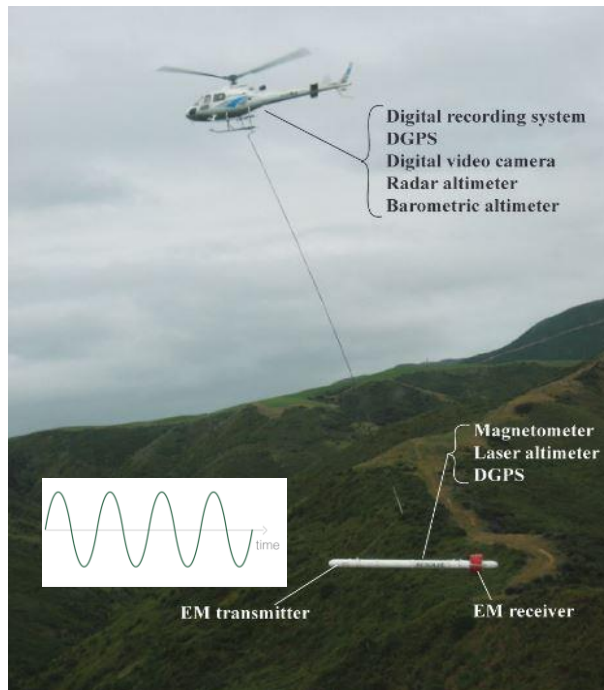

Horizontal Co-planar

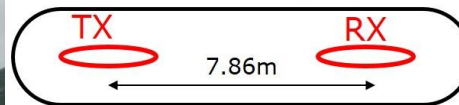

Vertical Co-axial

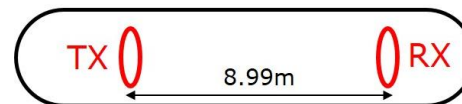



Horizontal Co-planar (HCP) frequencies:

- 382, 1822, 7970, 35920 and 130100 Hz

Vertical Co-axial (VCA) frequencies:

- 3258 Hz

VTEM (2007)

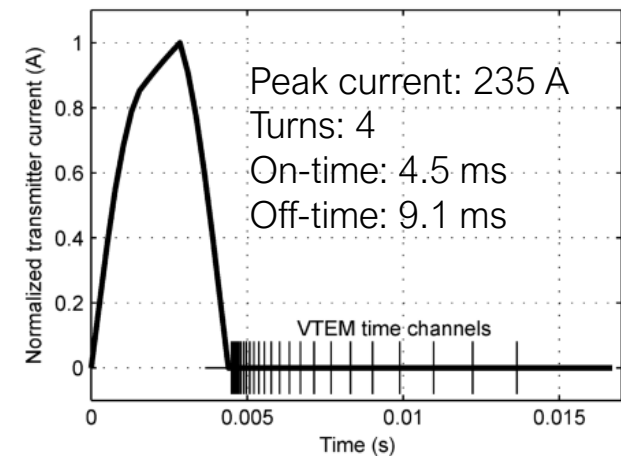
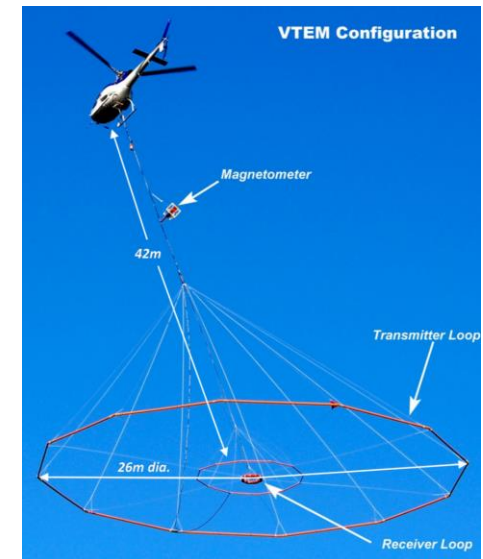


Horizontal Co-planar (HCP) data


In-Phase (Real)

Quadrature (Imaginary)



382 Hz

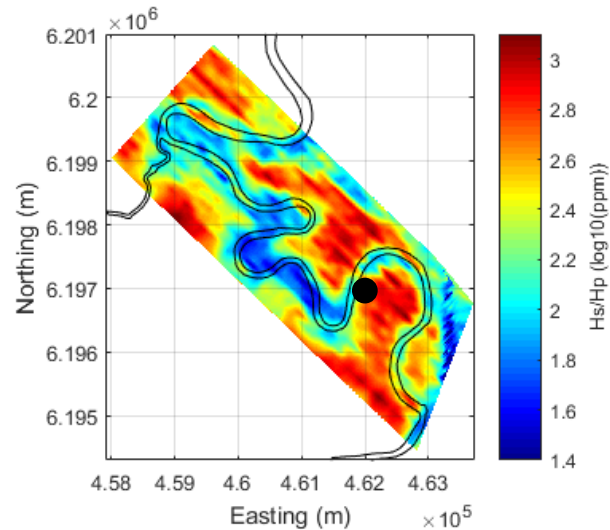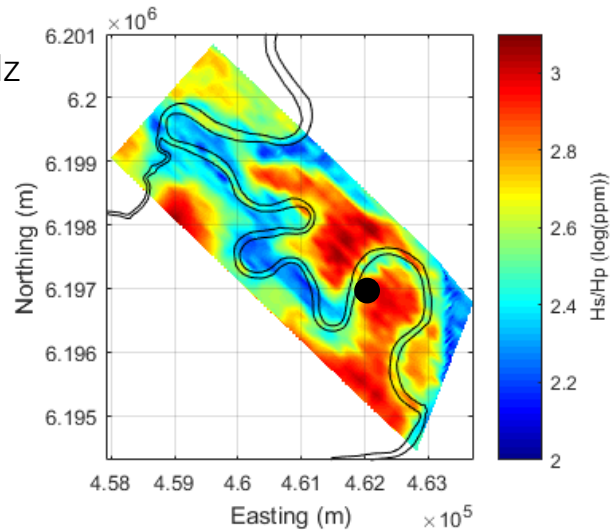


Sounding curve

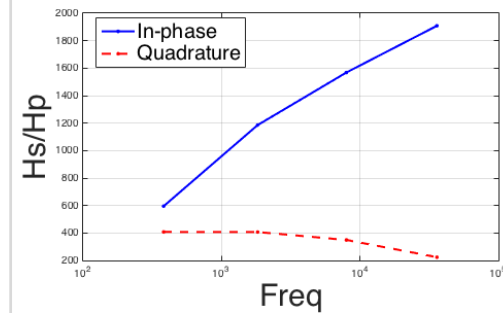



35920 Hz

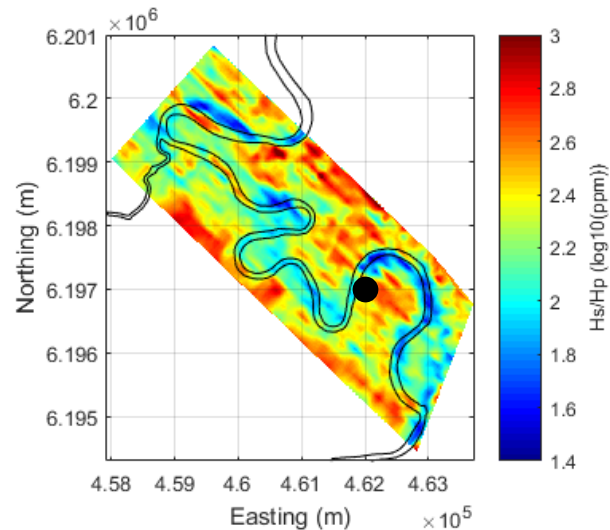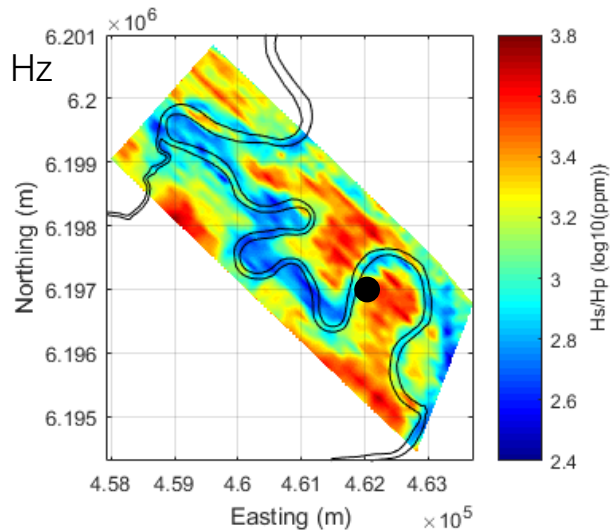

Response curve

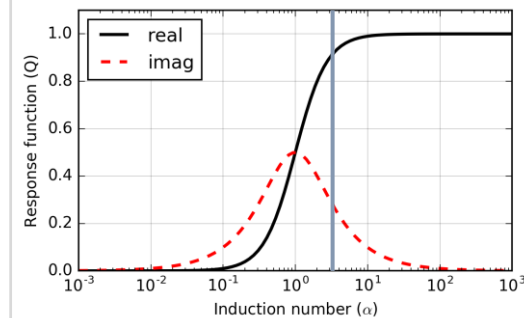

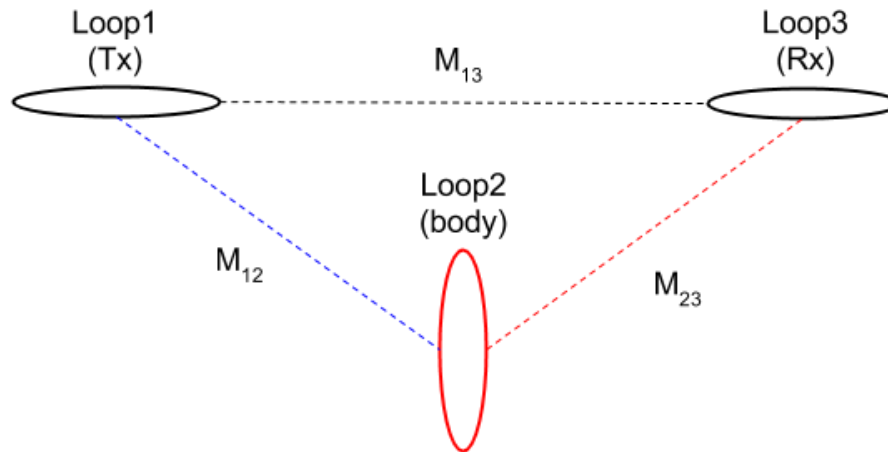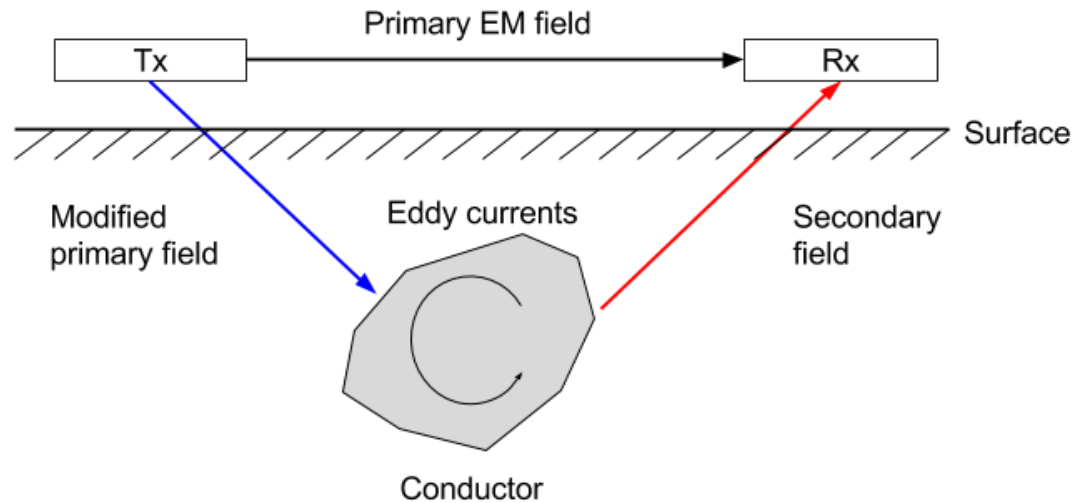Understand frequency domain EM induction using RL circuits



https://em.geosci.xyz/content/maxwell3_fdem/circuitmodel_for_eminduction/index.html

3-Loop system

- Suppose alternating current, $I_1 e^{i\omega t}$, is flowing in the Tx (Loop 1)
- This current generates an alternating magnetic field in the surrounding environment (e.g., the Earth's subsurface)
- which in turn induces an EMF both in the body (Loop 2) and the Rx (Loop 3)
- Recall that $\varepsilon_2 = -\frac{d\Phi_2}{dt} = -M_{12} \frac{dI_1}{dt}$
- Therefore,

$$\varepsilon_3^p = -i\omega M_{13} I_1 e^{i\omega t}$$


$$\varepsilon_2 = -i\omega M_{12} I_1 e^{i\omega t}$$

- What is the current in the body (Loop 2)?

$$I_2 = \frac{\varepsilon_2}{R + i\omega L} = -\frac{i\omega M_{12}}{R + i\omega L} I_1 e^{i\omega t}$$


- We are interested only in the secondary magnetic field that this current produces, and particularly the EMF induced in the Rx
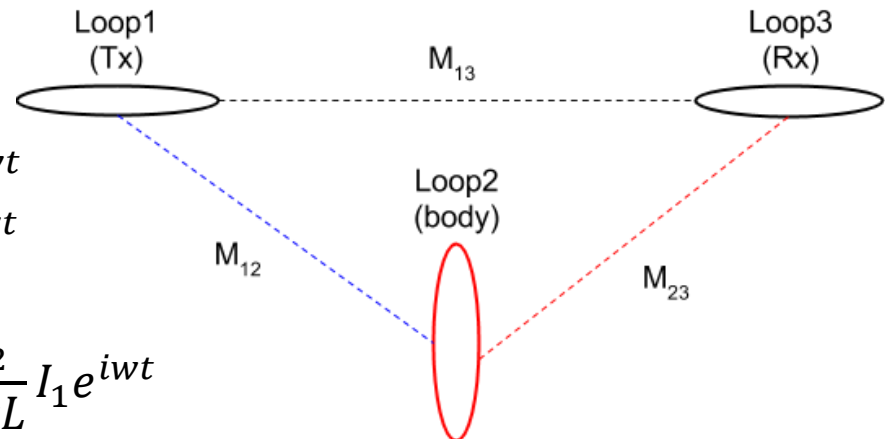
$$\varepsilon_3^s = -M_{23} \frac{dI_2}{dt} = -i\omega M_{23} I_2$$



https://em.geosci.xyz/content/maxwell3_fdem/circuitmodel_for_eminduction/derive_response_function.html

3-Loop system

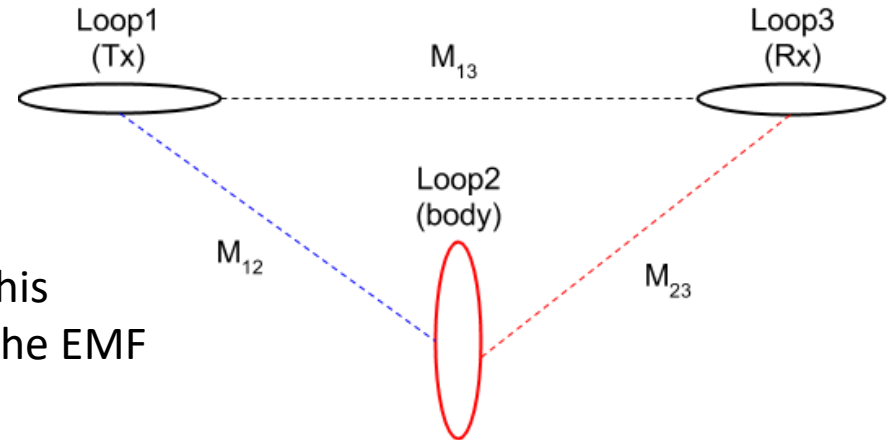

$$\varepsilon_3^p = -i\omega M_{13} I_1 e^{i\omega t}$$

$$\varepsilon_3^s = -M_{23} \frac{dI_2}{dt} = -i\omega M_{23} I_2$$


- In most cases, EM instrument measures this anomalous voltage by comparing it with the EMF induced by the primary field
- That is, it measures $\frac{\varepsilon_3^s}{\varepsilon_3^p}$

$$\begin{aligned} \frac{\varepsilon_3^s}{\varepsilon_3^p} &= \frac{i\omega M_{23} I_2}{i\omega M_{13} I_1 e^{i\omega t}} = \frac{M_{23} I_2}{M_{13} I_1 e^{i\omega t}} = \frac{M_{23} \left(-\frac{i\omega M_{12}}{R + i\omega L} I_1 e^{i\omega t} \right)}{M_{13} I_1 e^{i\omega t}} \\ &= -\frac{M_{12} M_{23}}{M_{13}} \frac{i\omega}{R + i\omega L} = -\frac{M_{12} M_{23}}{M_{13} L} \frac{i\omega L}{R + i\omega L} = -\frac{M_{12} M_{23}}{M_{13} L} \frac{\frac{i\omega L}{R}}{1 + \frac{i\omega L}{R}} = \\ &= -\frac{M_{12} M_{23}}{M_{13} L} \frac{i\alpha}{1 + i\alpha} = -\frac{M_{12} M_{23}}{M_{13} L} \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \end{aligned}$$

where $\alpha = \frac{\omega L}{R}$ is dimensionless and termed induction number.

https://em.geosci.xyz/content/maxwell3_fdem/circuitmodel_for_eminduction/derive_response_function.html

3-Loop system

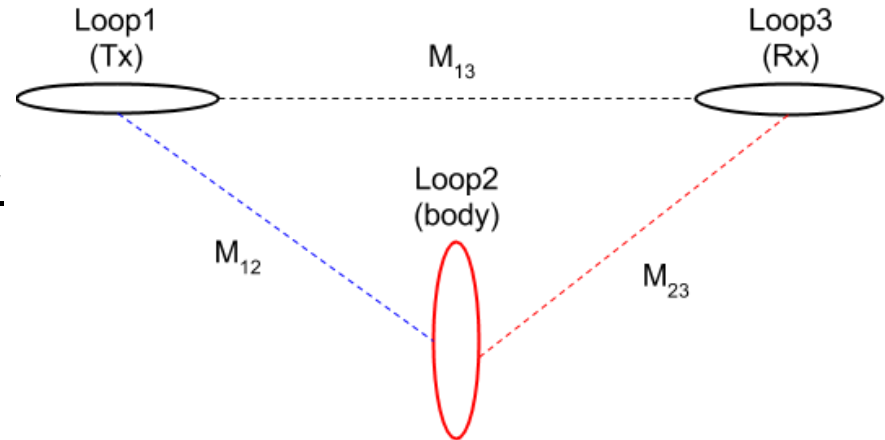

$$\frac{\varepsilon_3^s}{\varepsilon_3^p} = -\frac{M_{12}M_{23}}{M_{13}L} \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{where } \alpha = \frac{\omega L}{R}$$

$$\frac{\varepsilon_3^s}{\varepsilon_3^p} = CQ(\alpha)$$

$$C = -\frac{M_{12}M_{23}}{M_{13}L}$$

Coupling coefficient determined by geometry


$$Q = \frac{\alpha^2 + i\alpha}{1 + \alpha^2}$$

Response function relates to the target body

https://em.geosci.xyz/content/maxwell3_fdem/circuitmodel_for_eminduction/derive_response_function.html

How about magnetic field?

- We know that $\Phi_2 = M_{12}I_1$
- Suppose the loop is small enough that the magnetic field within it is uniform
- Then $\Phi_2 = BA$ where A is the area of the loop and B is one component of the induced magnetic field that depends on the coil orientation. For example, if coil is horizontal (parallel with the ground surface), then it measures the vertical component of the magnetic field. If it happens to align with the direction of the magnetic field, it measures the magnitude of the magnetic field.
- Thus, $B = \frac{M_{12}}{A} I_1$

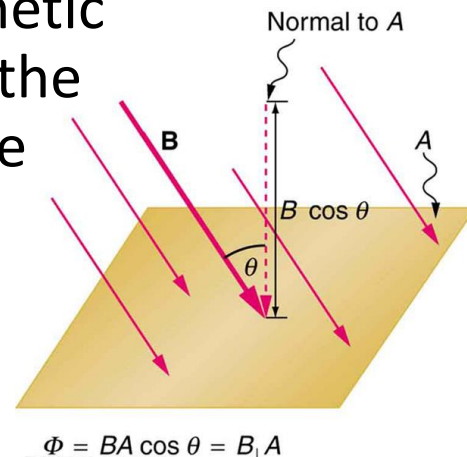

How about magnetic field?

- $B = \frac{M_{12}}{A} I_1$

- Therefore,

$$B_p^3 = \frac{M_{13}}{A} I_1$$


$$B_s^3 = \frac{M_{23}}{A} I_2$$

- Therefore,

$$\frac{B_s^3}{B_p^3} = \frac{M_{23} I_2}{M_{13} I_1} = \frac{M_{23} \left(-\frac{i\omega M_{12}}{R+i\omega L} I_1 e^{i\omega t} \right)}{M_{13} I_1 e^{i\omega t}} = -\frac{M_{12} M_{23}}{M_{13}} \frac{i\omega}{R+i\omega L} = -\frac{M_{12} M_{23}}{M_{13} L} \frac{\alpha^2 + i\alpha}{1 + \alpha^2} = \frac{\varepsilon_3^s}{\varepsilon_3^p}$$

Similarly, $\frac{H_s^3}{H_p^3} = \frac{\varepsilon_3^s}{\varepsilon_3^p} = CQ(\alpha)$

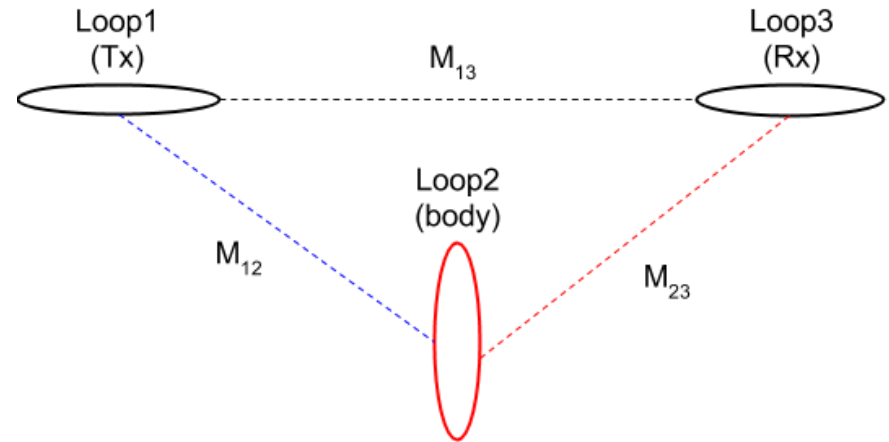- Therefore, the fields and the voltages can be used interchangeably when measured with a coil.




This is what we have learned so far

$$\frac{H_s^3}{H_p^3} = \frac{\epsilon_3^s}{\epsilon_3^p} = CQ(\alpha)$$

$$C = -\frac{M_{12}M_{23}}{M_{13}L} \quad \text{Coupling coefficient}$$


$$Q = \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{Response function}$$

Coupling between loops

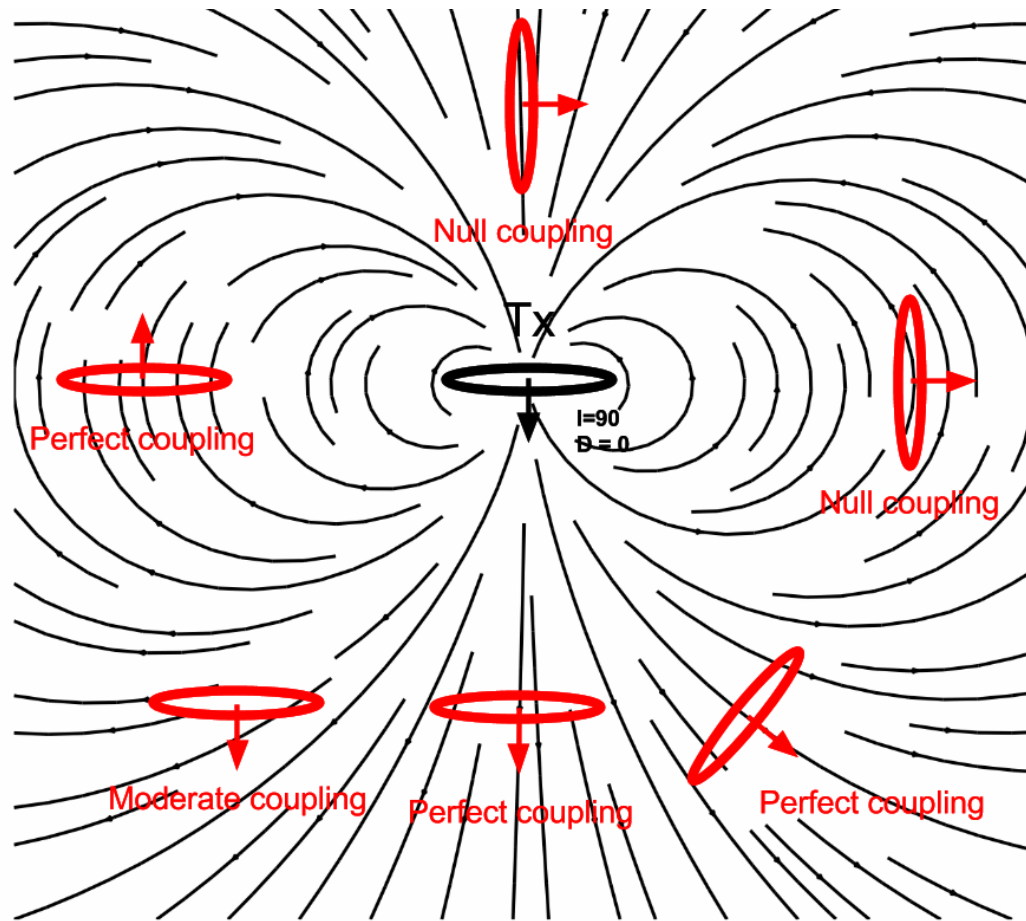

https://em.geosci.xyz/content/maxwell3_fdem/circuitmodel_for_eminduction/understanding_harmonicEMresponse.html

Response function

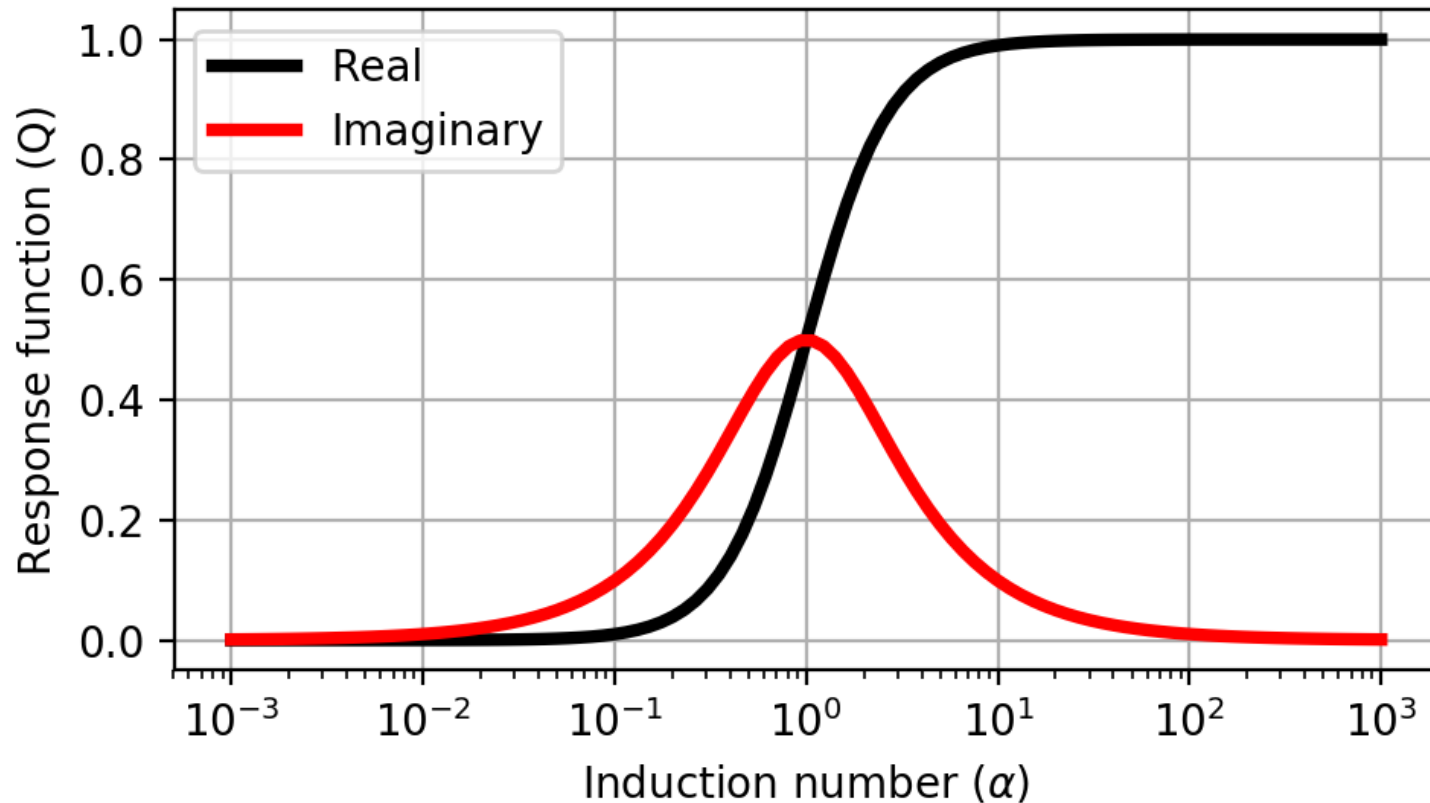

https://em.geosci.xyz/content/maxwell3_fdem/circuitmodel_for_eminduction/derive_response_function.html


Understanding the response function

$$Q = \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{with } \alpha = \frac{\omega L}{R}$$

when $\alpha \ll 1$

$$Q \approx i\alpha$$

- The EM response is purely imaginary and small.
- The amount of current induced in the body will also be small. Remember that $|I| = \frac{\varepsilon_2}{\sqrt{R^2 + \omega^2 L^2}}$

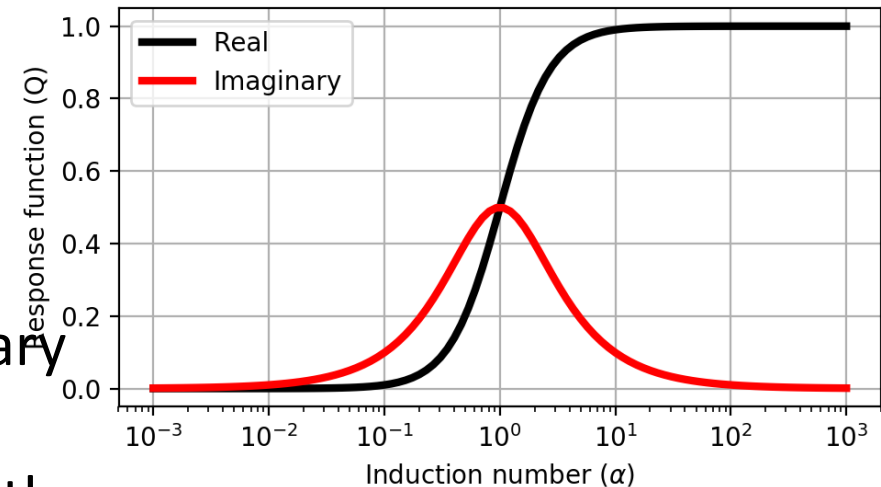


Understanding the response function

$$Q = \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{with } \alpha = \frac{\omega L}{R}$$

Resistive limit: when $\alpha \ll 1$

$$Q \approx i\alpha$$

- The EM response is purely imaginary and small.
- The amount of current induced in the body will also be small. Remember that $|I| = \frac{\varepsilon_2}{\sqrt{R^2 + \omega^2 L^2}}$

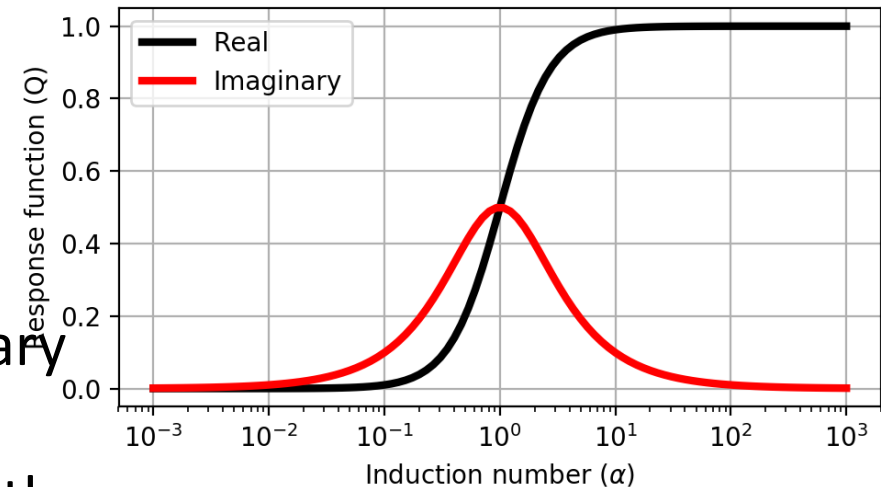


Understanding the response function

$$Q = \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{with } \alpha = \frac{\omega L}{R}$$

when $\alpha \gg 1$

$$Q \approx 1$$

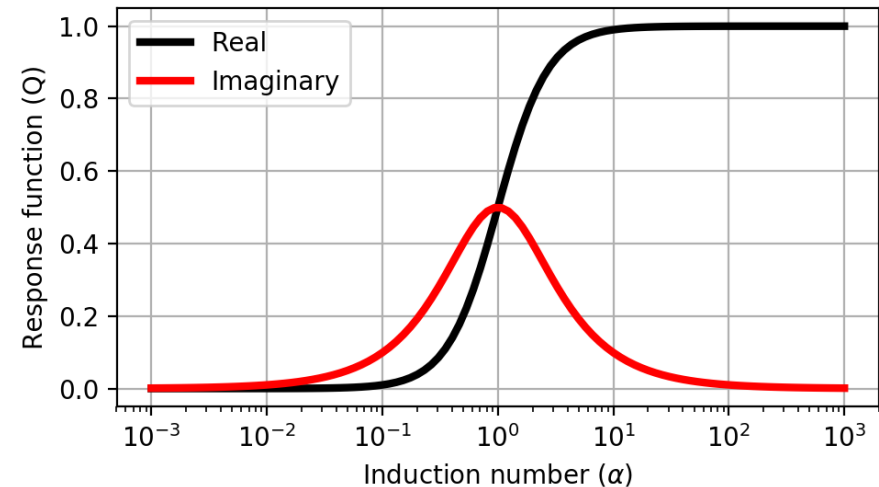- The EM response is largely real-valued.
- The imaginary part is very small.




Understanding the response function

$$Q = \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{with } \alpha = \frac{\omega L}{R}$$

Inductive limit: when $\alpha \gg 1$

$$Q \approx 1$$

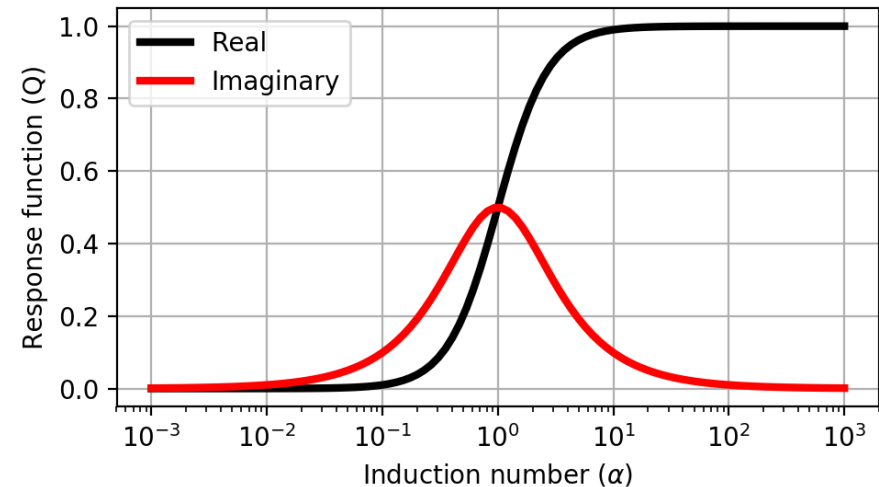- The EM response is largely real-valued.
- The imaginary part is very small.





Horizontal Co-planar (HCP) data


In-Phase (Real)

Quadrature (Imaginary)



382 Hz

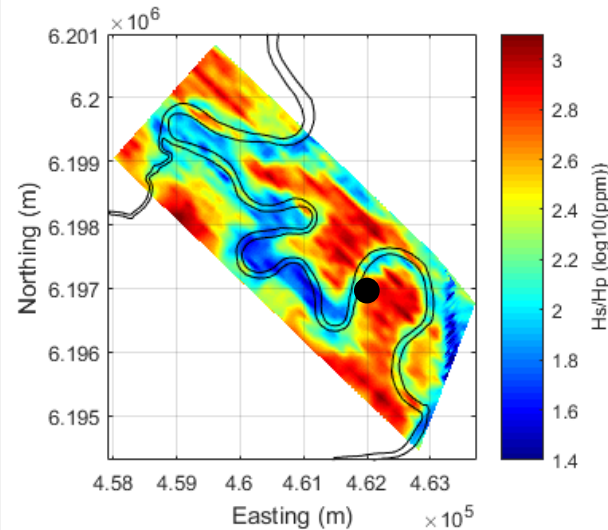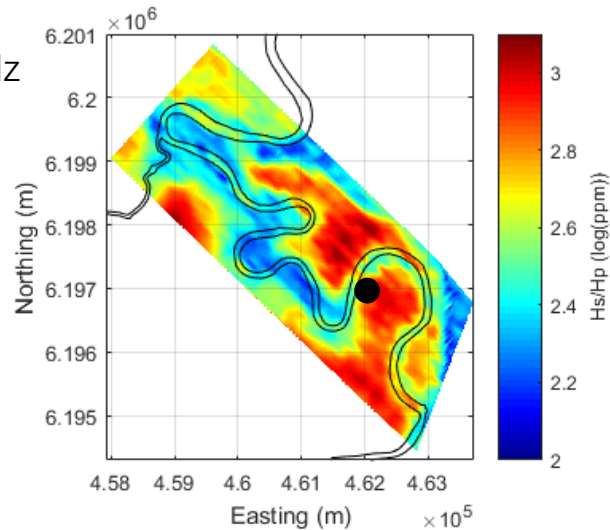


Sounding curve

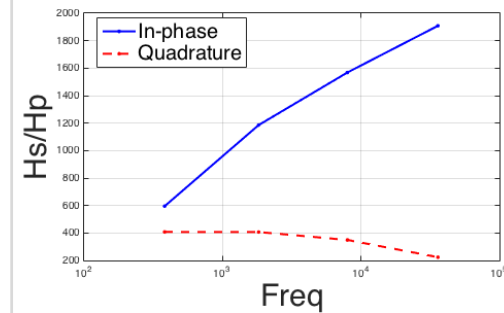

35920 Hz

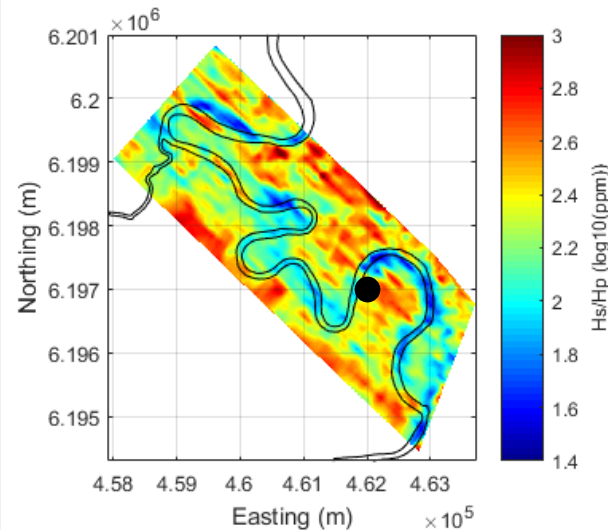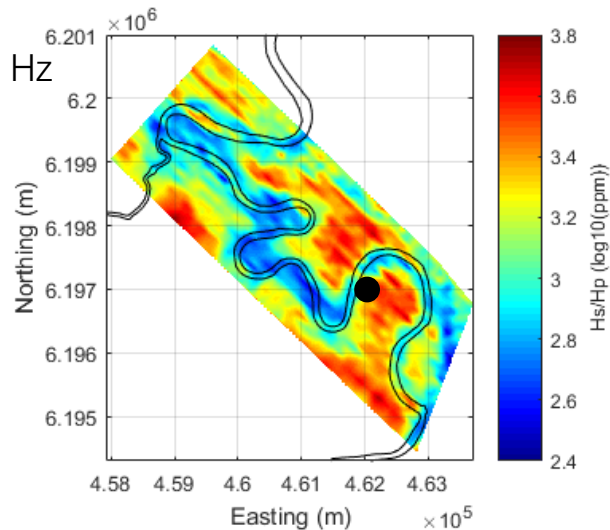

Response curve

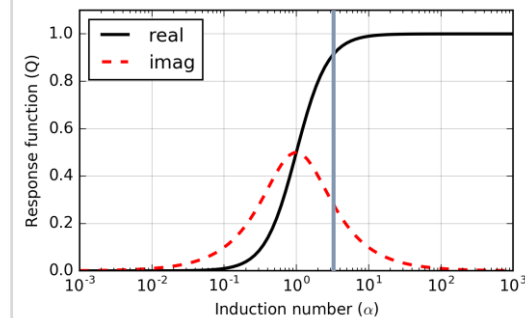

Understanding the harmonic EM response (optional)

$$\frac{H_s^3}{H_p^3} = -\frac{M_{12}M_{23}}{M_{13}L} \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{with } \alpha = \frac{\omega L}{R}$$

The phase:

$$\tan(\theta) = \frac{1}{\alpha}$$

How to obtain ϕ ?

From $\tan(\theta) = \frac{1}{\alpha}$, we obtain $\cot(\theta) = \alpha$


which is equal to $\tan(\frac{\pi}{2} - \theta) = \alpha$

Therefore, $\frac{\pi}{2} - \theta \pm k\pi = \tan^{-1}(\frac{\omega L}{R})$. Therefore, $\theta = \frac{\pi}{2} - \tan^{-1}(\frac{\omega L}{R}) \pm k\pi$

We know that θ must be negative, because we know that the secondary magnetic field lags behind the primary field. But in the meantime, $\tan(\theta)$ must be positive.

That leaves us with $-\pi < \theta < -\frac{\pi}{2}$.

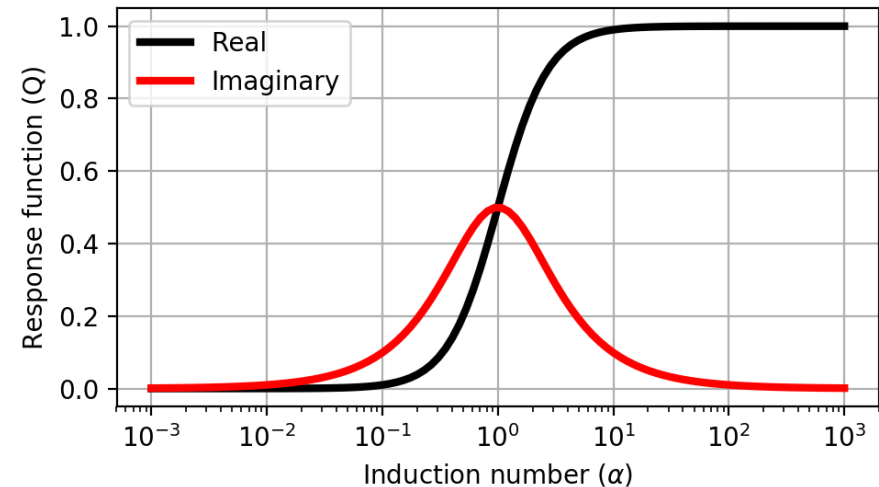Therefore, $\theta = \frac{\pi}{2} - \tan^{-1}(\frac{\omega L}{R}) - \pi = -\frac{\pi}{2} - \tan^{-1}(\frac{\omega L}{R})$




Understanding the harmonic EM response (optional)

$$\frac{H_s^3}{H_p^3} = -\frac{M_{12}M_{23}}{M_{13}L} \frac{\alpha^2 + i\alpha}{1 + \alpha^2} \quad \text{with } \alpha = \frac{wL}{R}$$

The phase:
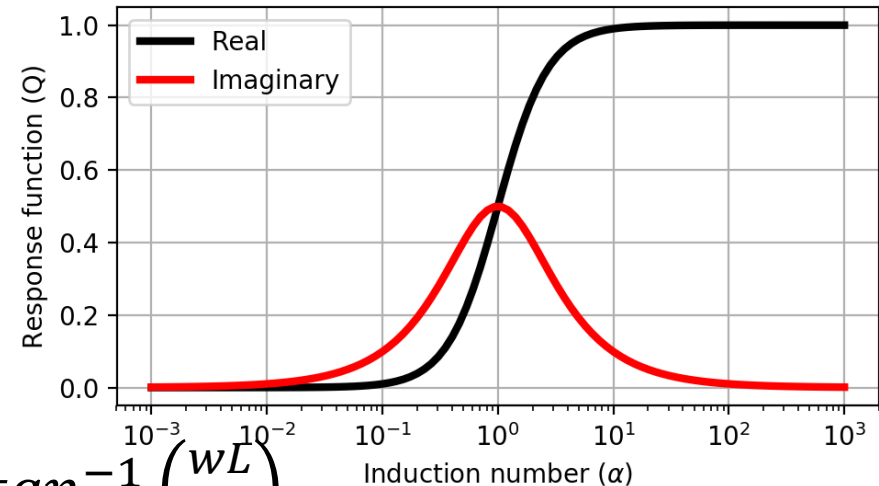
$$\tan(\theta) = \frac{1}{\alpha}$$
$$\theta = -\frac{\pi}{2} - \tan^{-1}\left(\frac{wL}{R}\right)$$



The phase lag is therefore, $\psi = \frac{\pi}{2} + \tan^{-1}\left(\frac{wL}{R}\right)$

The lag of $\frac{\pi}{2}$ is due to the inductive coupling between Loop 1 and Loop 2 (i.e., time-varying magnetic field induces EMF in Loop 2), whereas the additional phase lag $\tan^{-1}\left(\frac{wL}{R}\right)$ comes from the fact that Loop 2 is acting as a RL circuit when applied to an EMF.

For a very good conductor, $\frac{wL}{R} \rightarrow \infty$, $\psi \rightarrow \pi$. The phase of secondary field is 180° behind the primary field. For a very good resistor, the phase lag is 90°.

In-phase vs Out-of-phase

- Phase lag $\psi = \frac{\pi}{2} + \tan^{-1} \left(\frac{wL}{R} \right) = \frac{\pi}{2} + \phi$

$$H_s^3 = |H_s^3| \cos \left(wt - \left(\frac{\pi}{2} + \phi \right) \right)$$
$$= |H_s^3| \left(\cos \left(wt - \frac{\pi}{2} \right) \cos(\phi) + \cos(wt - \pi) \sin(\phi) \right)$$

The component of H_s^3 that is 180° out of phase with H^p is $|H_s^3| \sin(\phi)$. This is called **Real** or **In-phase** component.

The component 90° out of phase is $|H_s^3| \cos(\phi)$. This is called **Imaginary**, **Out-of-phase**, or **quadrature** component.

Understand time domain EM induction using RL circuits

Synthetic airborne TEM data


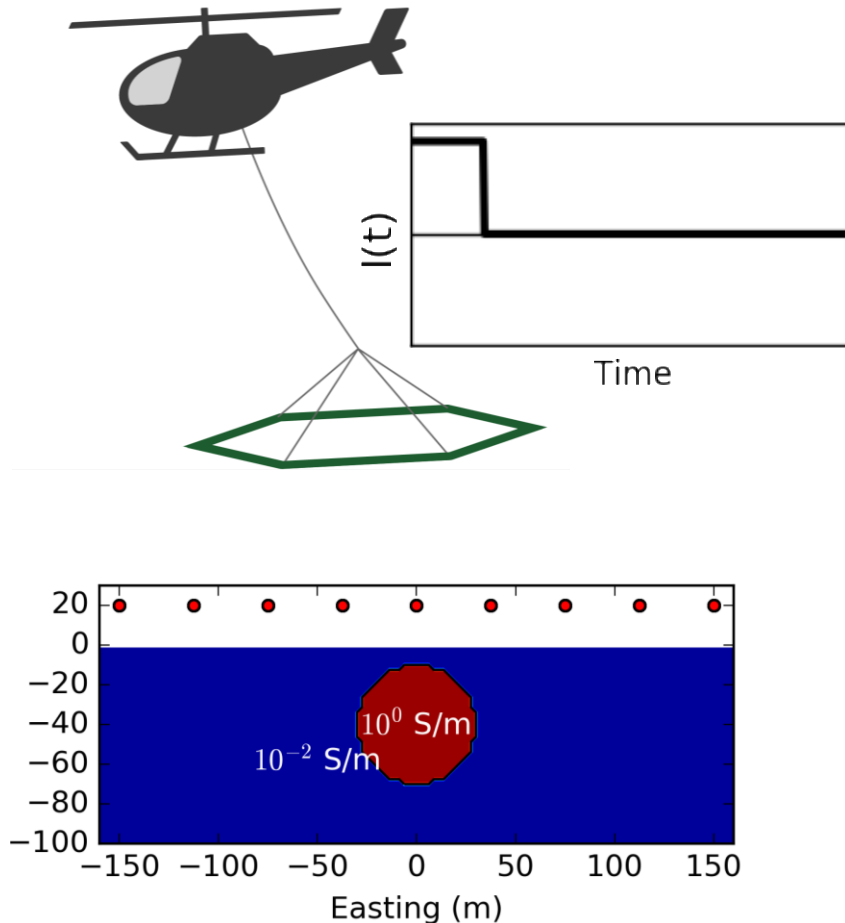



Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF

Data profile

Profile: N=0 m , Time: 0.025 ms

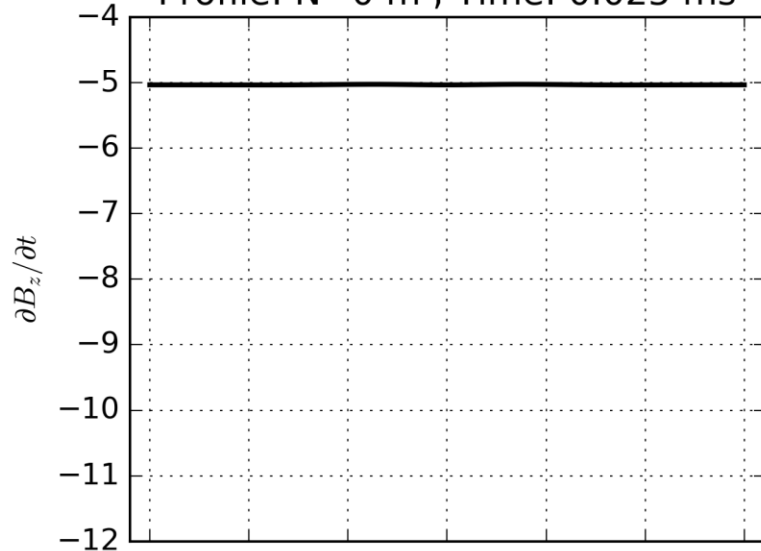

Data map

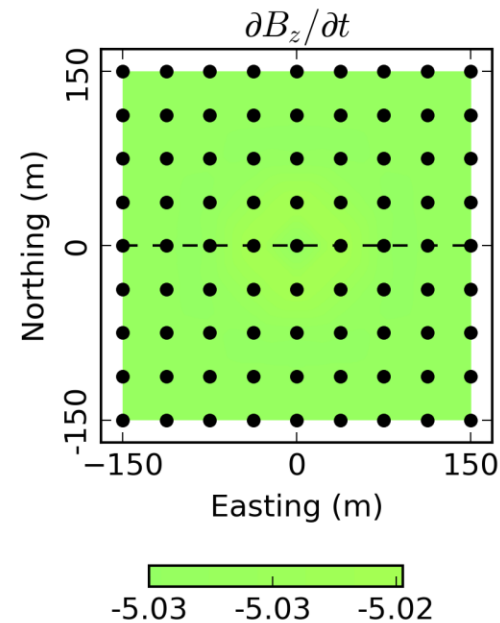

Conductivity


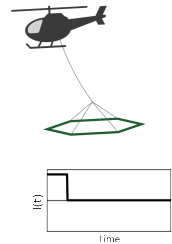
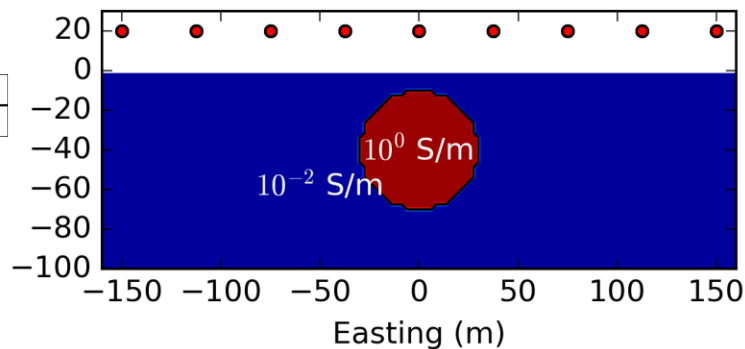



Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF

Data profile

Profile: N=0 m , Time: 0.045 ms

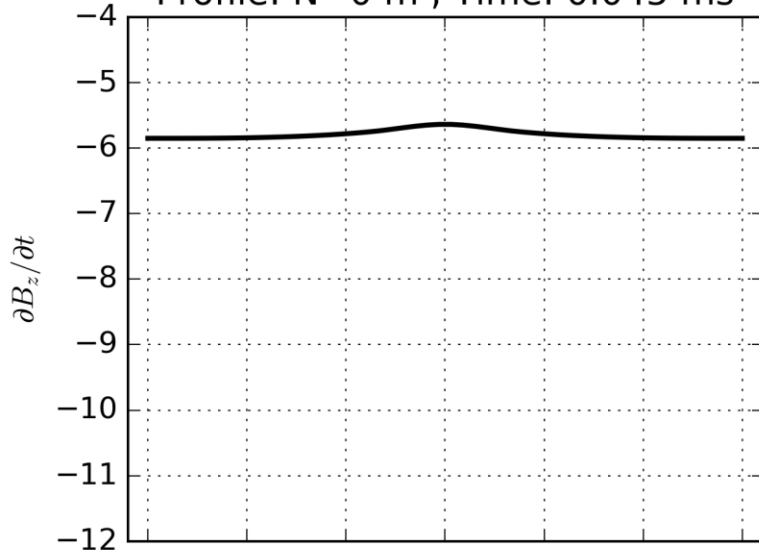

Data map

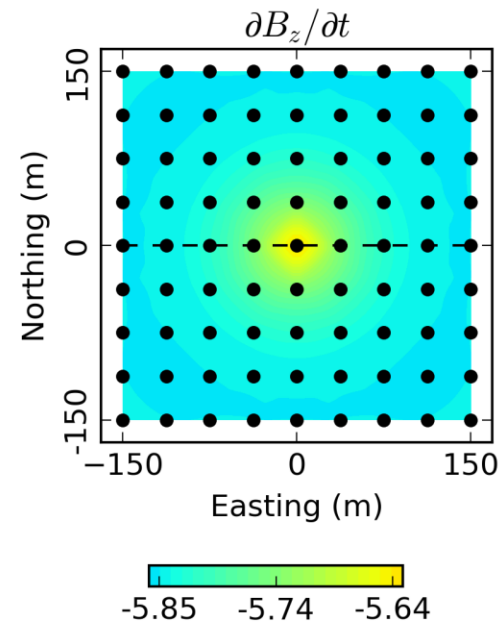

Conductivity


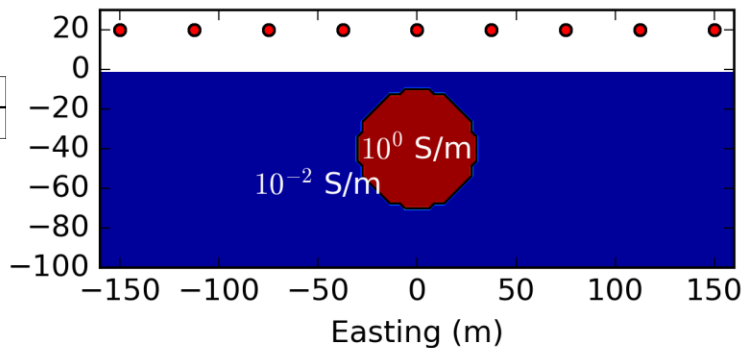



Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF

Data profile

Profile: N=0 m , Time: 0.305 ms

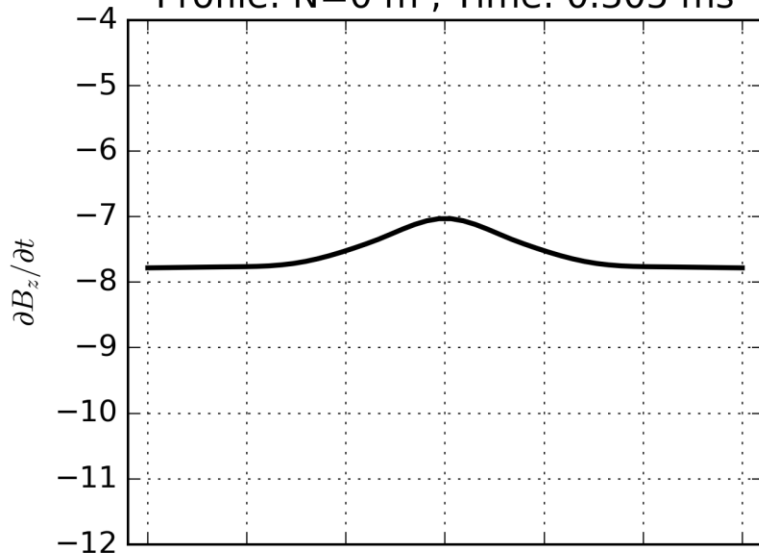

Data map

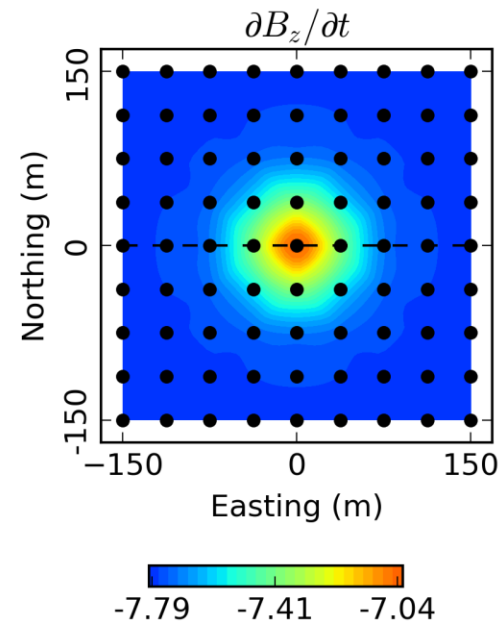

Conductivity


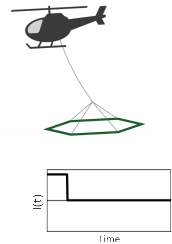
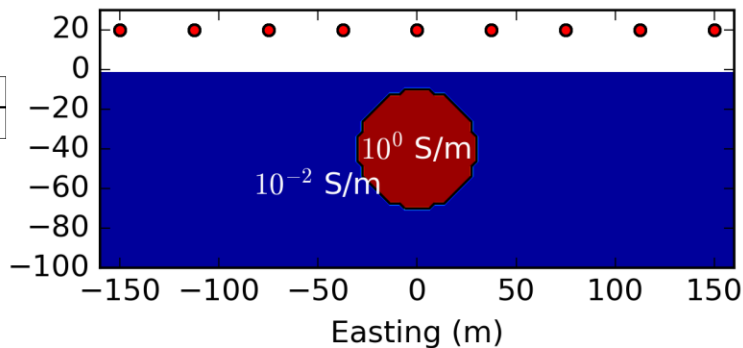



Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF

Data profile

Profile: N=0 m , Time: 0.905 ms

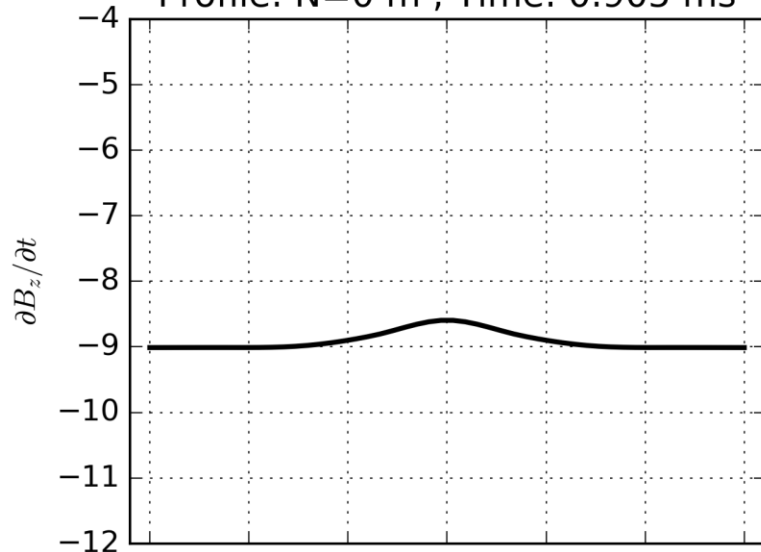

Data map

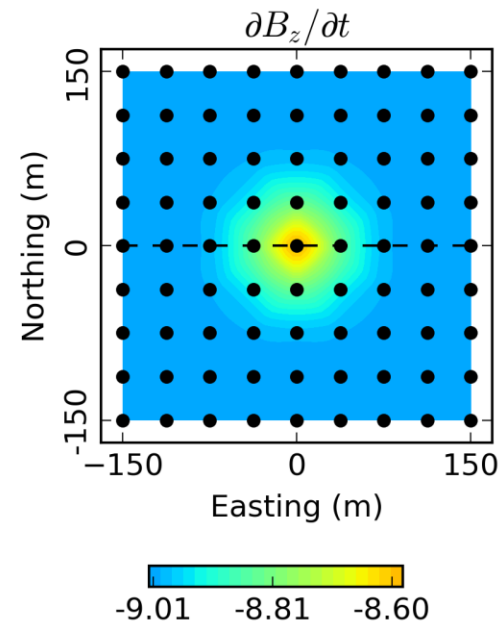

Conductivity


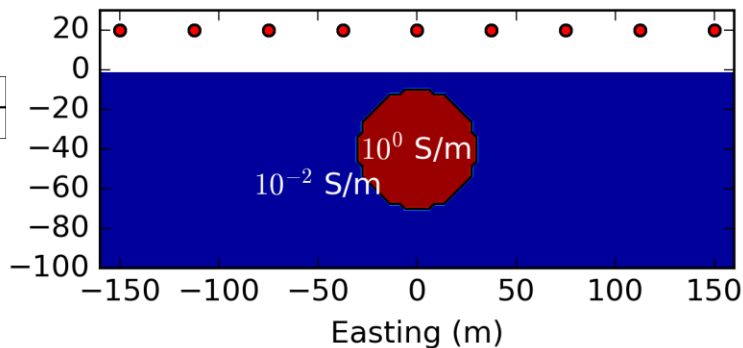



Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF

Data profile

Profile: N=0 m , Time: 4.005 ms

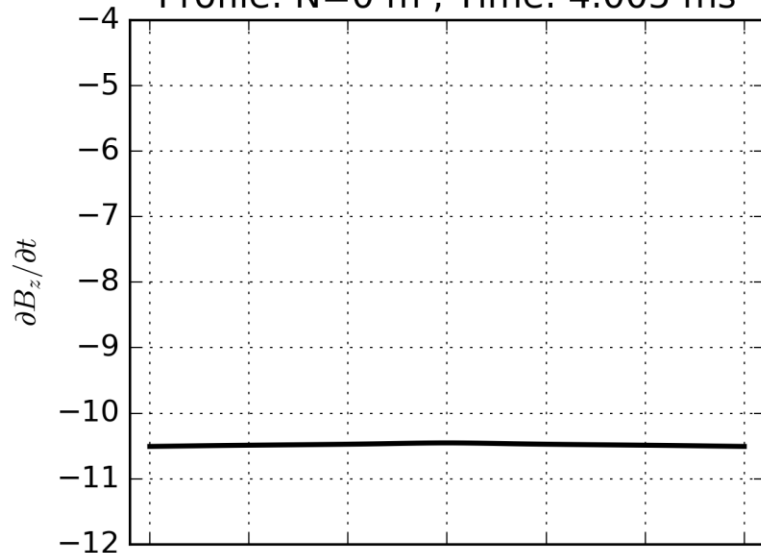

Data map

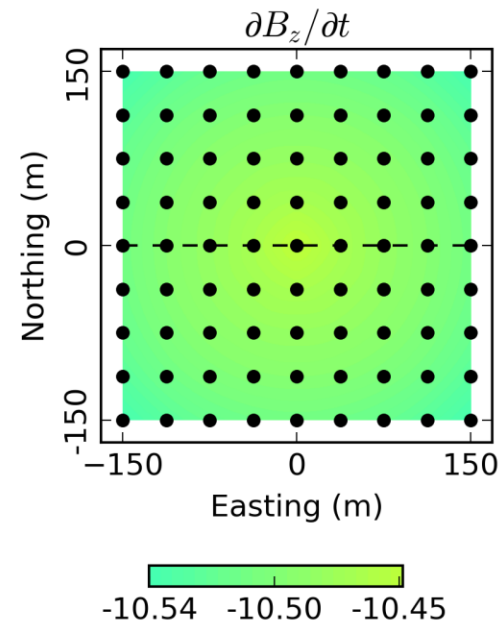

Conductivity

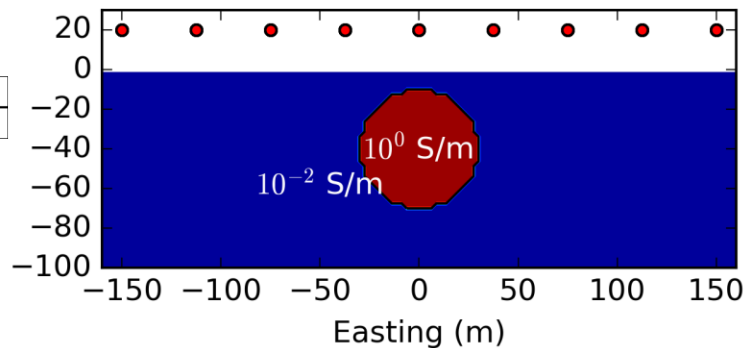


Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF

Synthetic airborne TEM data


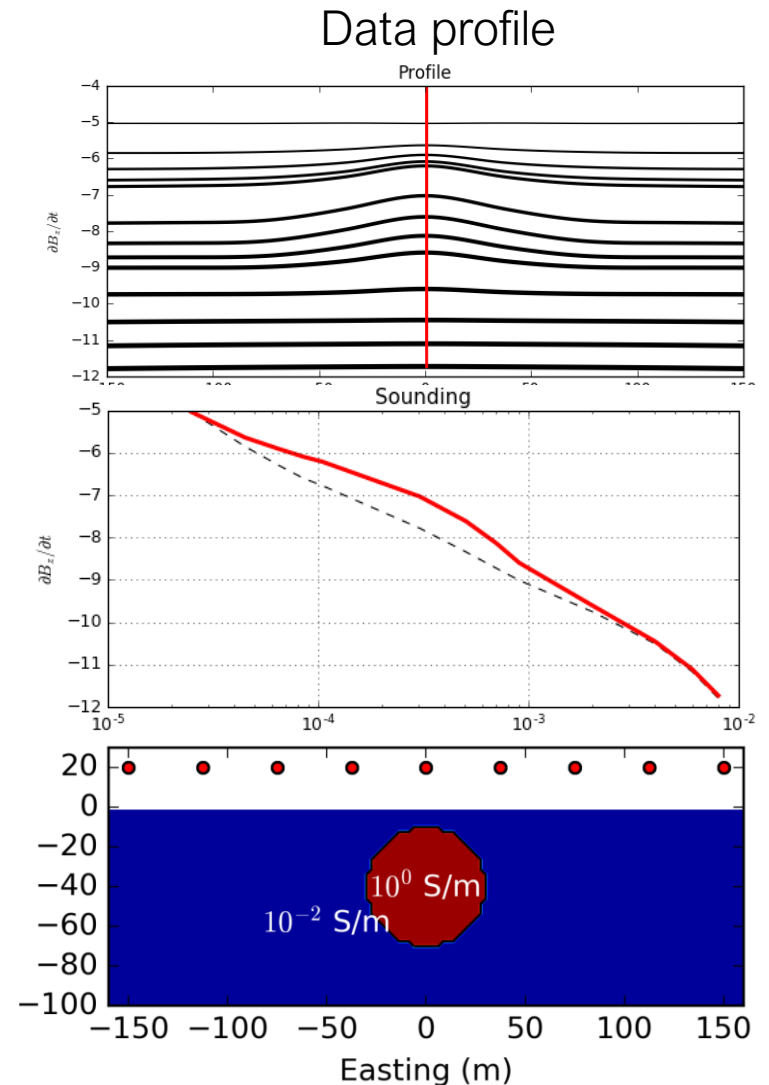
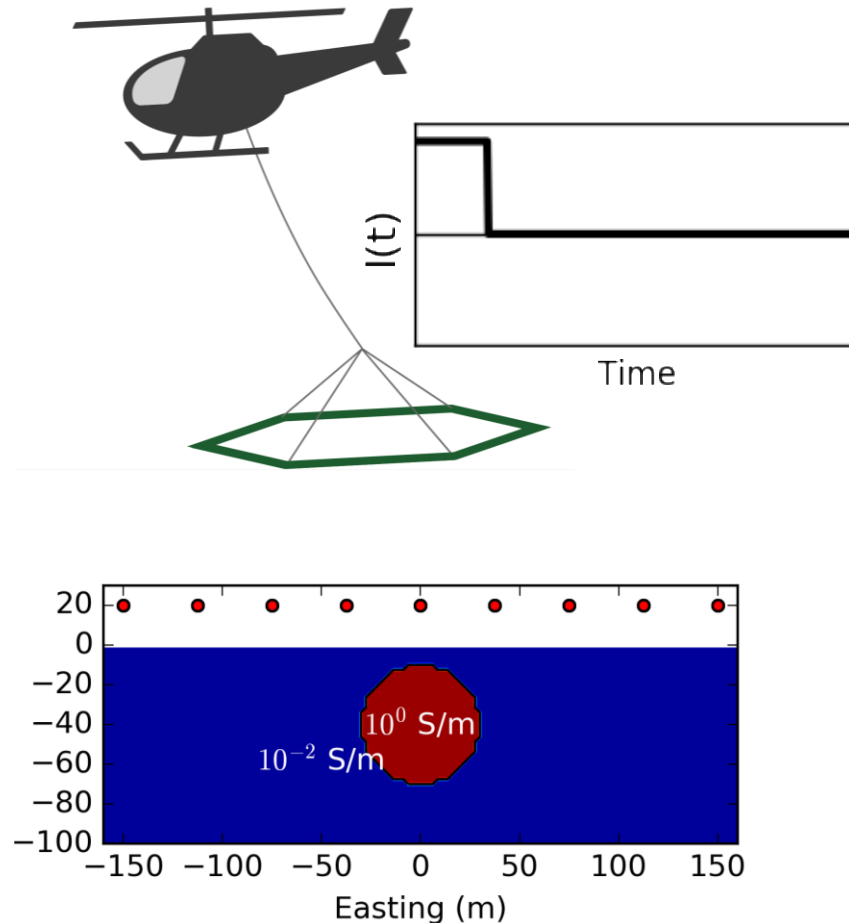
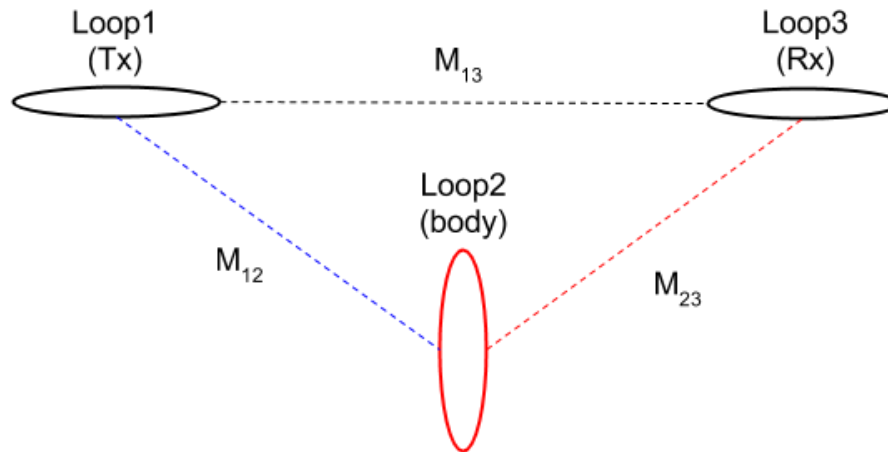



Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF

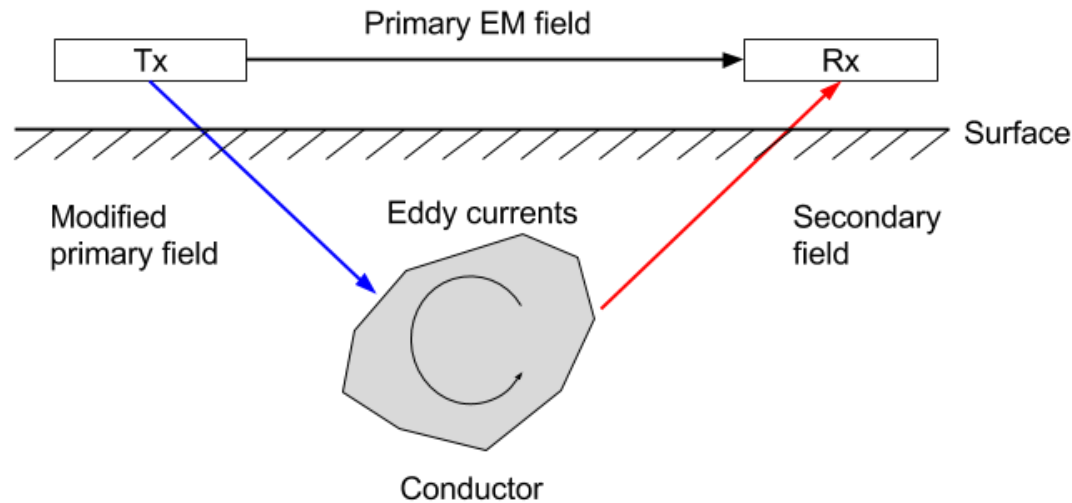

https://em.geosci.xyz/content/maxwell3_fdem/circuitmodel_for_eminduction/index.html

Step-off current

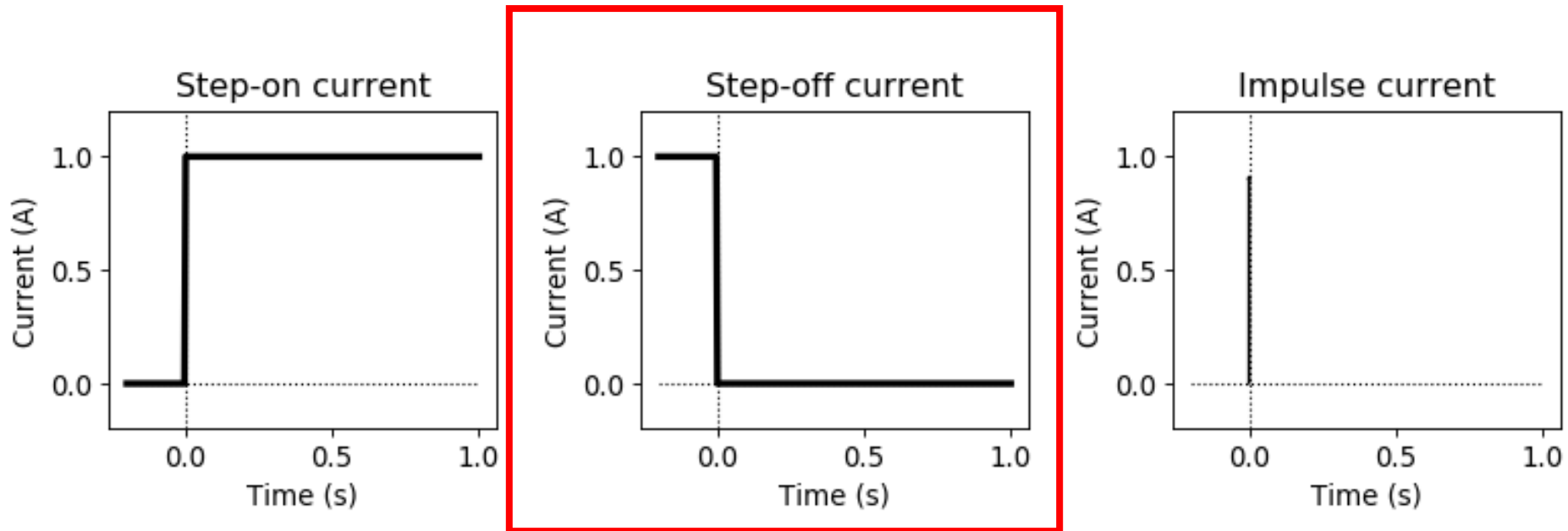- Let us consider a step-off current in the transmitter



- Mathematically, $I(t) = I_1(1 - u(t))$, where $u(t)$ is Heaviside step function.


Primary voltage in Loop 3

- The magnetic flux through Loop 3 is

$$\Phi_{13} = M_{13}I(t) = M_{13}I_1(1 - u(t))$$

- Thus, the primary voltage is
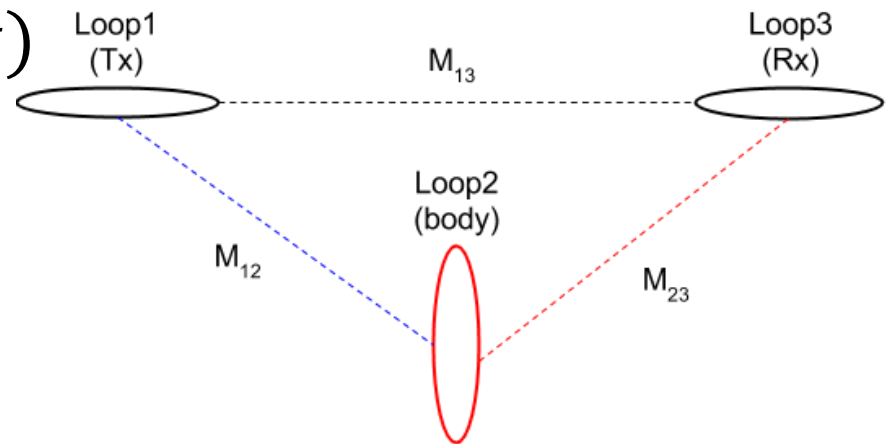
$$\varepsilon_3^P = -\frac{\partial \Phi_{13}}{\partial t} = M_{13}I_1\delta(t)$$




EMF in Loop 2

- What is the EMF in Loop 2 due to the step-off current in Loop 1?

$$\Phi_{12} = M_{12}I(t) = M_{12}I_1(1 - u(t))$$
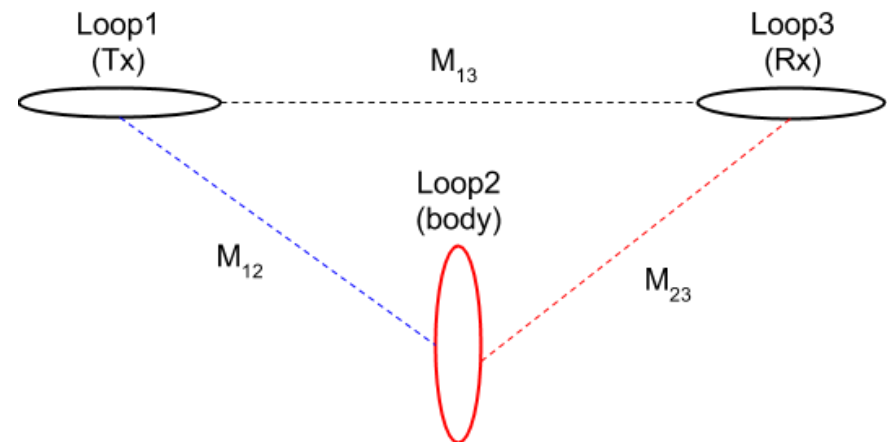
$$\varepsilon_2 = -\frac{\partial \Phi_{12}}{\partial t} = M_{12}I_1\delta(t)$$



How about current in Loop 2?



- Consider Loop 2 as a RL circuit
- Applying KVL, we have

$$\varepsilon_2 - L \frac{dI_2(t)}{dt} - I_2(t)R = 0$$

- Solving the above equation, we obtain

$$I_2(t) = \frac{M_{12}I_1}{L} e^{-t/\tau}, (t > 0)$$
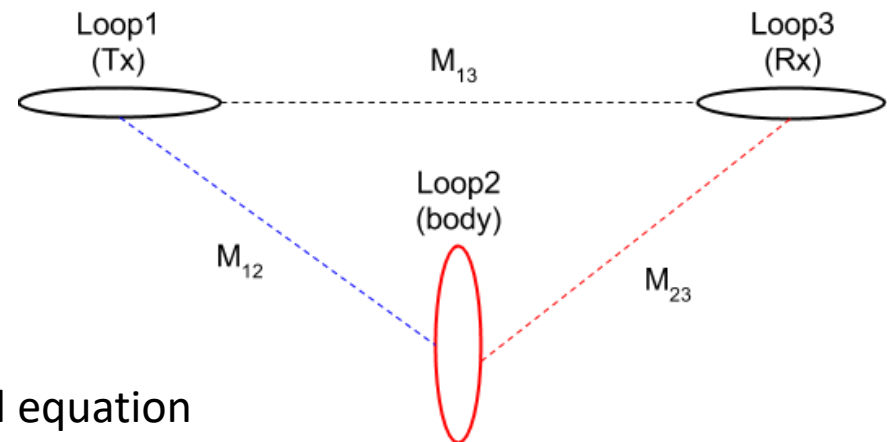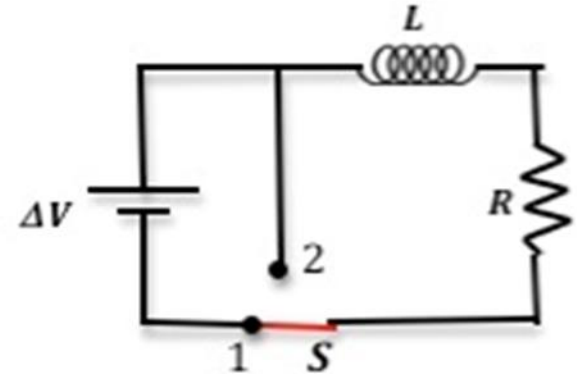
$$\text{time constant } \tau = \frac{L}{R}$$



See next slide for how to solve the differential equation

Calculate current in Loop 2 (Optional)

Applying KVL, we have

$$\varepsilon_2 - L \frac{dI_2(t)}{dt} - I_2(t)R = 0$$

Remember

$$\varepsilon_2 = -\frac{\partial \Phi_{12}}{\partial t} = M_{12}I_1\delta(t)$$

Therefore,

$$M_{12}I_1\delta(t) = L \frac{dI_2(t)}{dt} + I_2(t)R$$

Apply Fourier transform to both sides

$$\begin{aligned}\mathcal{F}[\delta(t)] &= 1 \\ \mathcal{F}[I_2(t)] &= \tilde{I}_2(\omega)\end{aligned}$$

Therefore,

$$M_{12}I_1 = L \cdot i\omega \cdot \tilde{I}_2(\omega) + \tilde{I}_2(\omega)R$$

It then follows that,

$$\tilde{I}_2(\omega) = \frac{M_{12}I_1}{R + i\omega L}$$

In order to get $I_2(t)$, apply the inverse Fourier transform

$$I_2(t) = \mathcal{F}^{-1}[\tilde{I}_2(\omega)] = \mathcal{F}^{-1}\left[\frac{M_{12}I_1}{R + i\omega L}\right]$$

Note that

$\mathcal{F}[e^{-at}u(t)] = \frac{1}{a+i\omega}$, where $u(t)$ is Heaviside step function

$$\text{Thus, } \mathcal{F}^{-1}\left[\frac{1}{a+i\omega}\right] = e^{-at}u(t)$$


Therefore,

$$I_2(t) = \mathcal{F}^{-1}\left[\frac{M_{12}I_1}{R+i\omega L}\right] = M_{12}I_1 \cdot \mathcal{F}^{-1}\left[\frac{1}{L} \cdot \frac{1}{\frac{1}{\tau} + i\omega}\right] =$$

$$\frac{M_{12}I_1 e^{-\frac{t}{\tau}}}{L} u(t) = \frac{M_{12}I_1}{L} e^{-t/\tau}, (t > 0), \text{ where } \tau = \frac{L}{R}$$

Secondary voltage in Loop 3

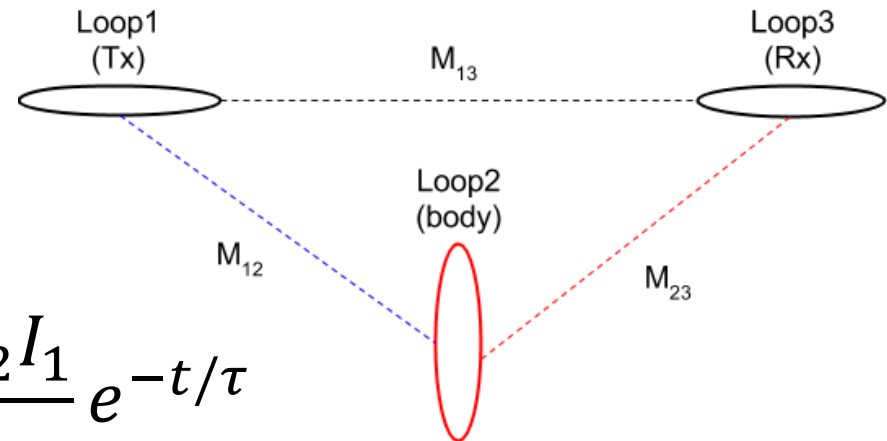- Now that we have obtained the current in Loop 3, how about the secondary EMF in Loop 3?






$$\Phi_{23} = M_{23}I_2(t) = M_{23} \frac{M_{12}I_1}{L} e^{-t/\tau}$$

$$\varepsilon_3^s = -\frac{\partial \Phi_{23}}{\partial t} = \frac{M_{12}M_{23}}{L} \frac{I_1}{\tau} e^{-t/\tau}, t > 0$$

Secondary voltage in Loop 3
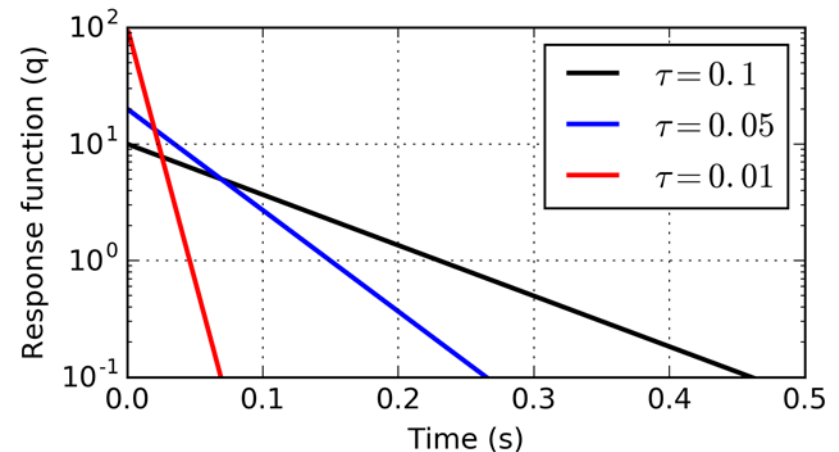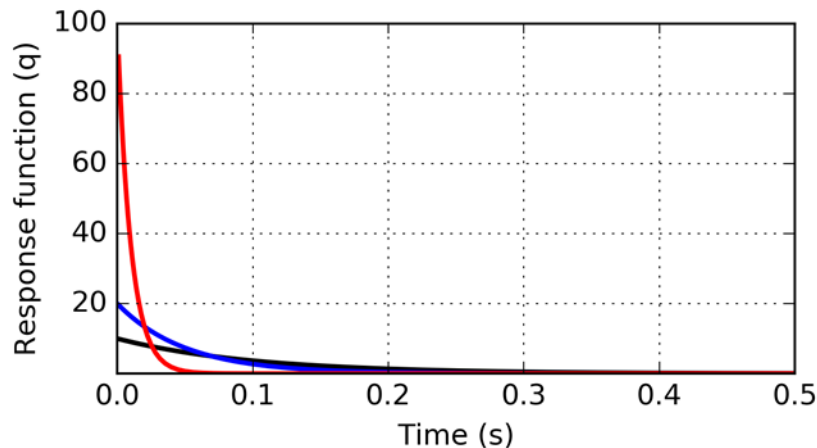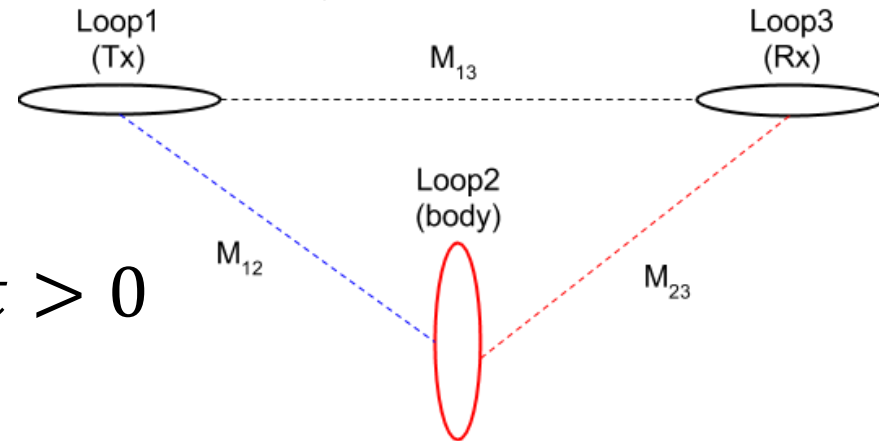
$$\varepsilon_3^s = -\frac{\partial \Phi_{23}}{\partial t} = \frac{M_{12}M_{23}}{L} \frac{I_1}{\tau} e^{-t/\tau}, t > 0$$



The larger the τ , the slower it decays. Remember $\tau = \frac{L}{R}$.

Therefore, the more conductive the subsurface, the slower it decays.

Synthetic airborne TEM data

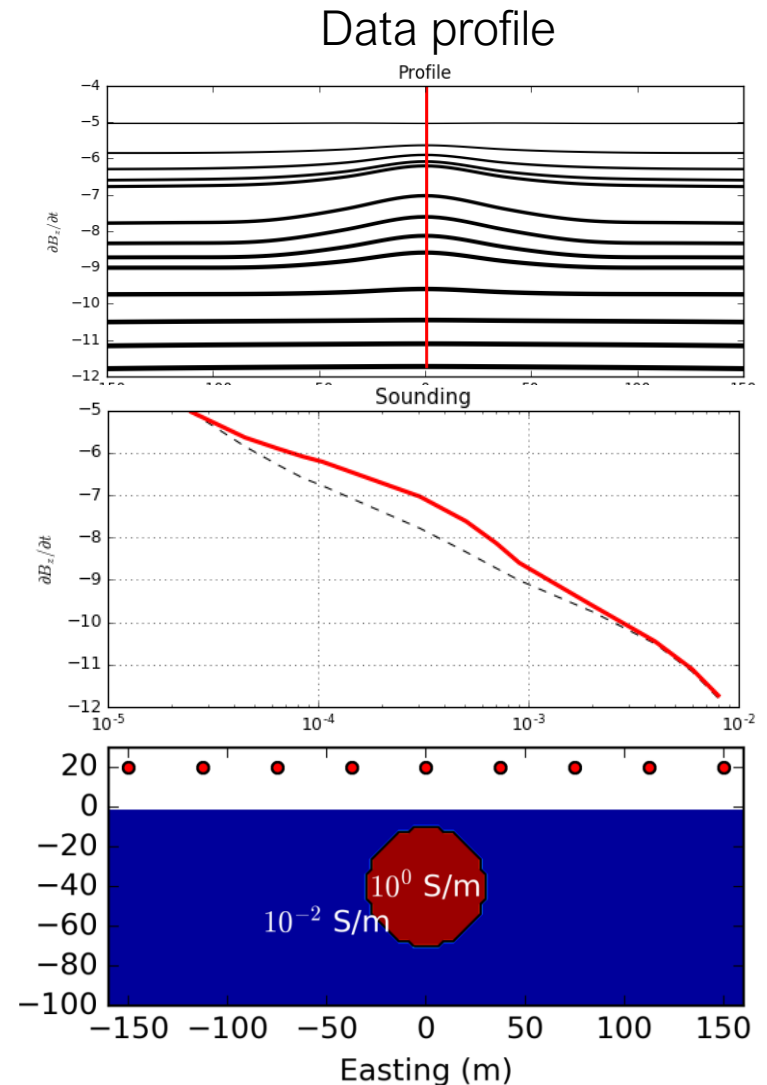
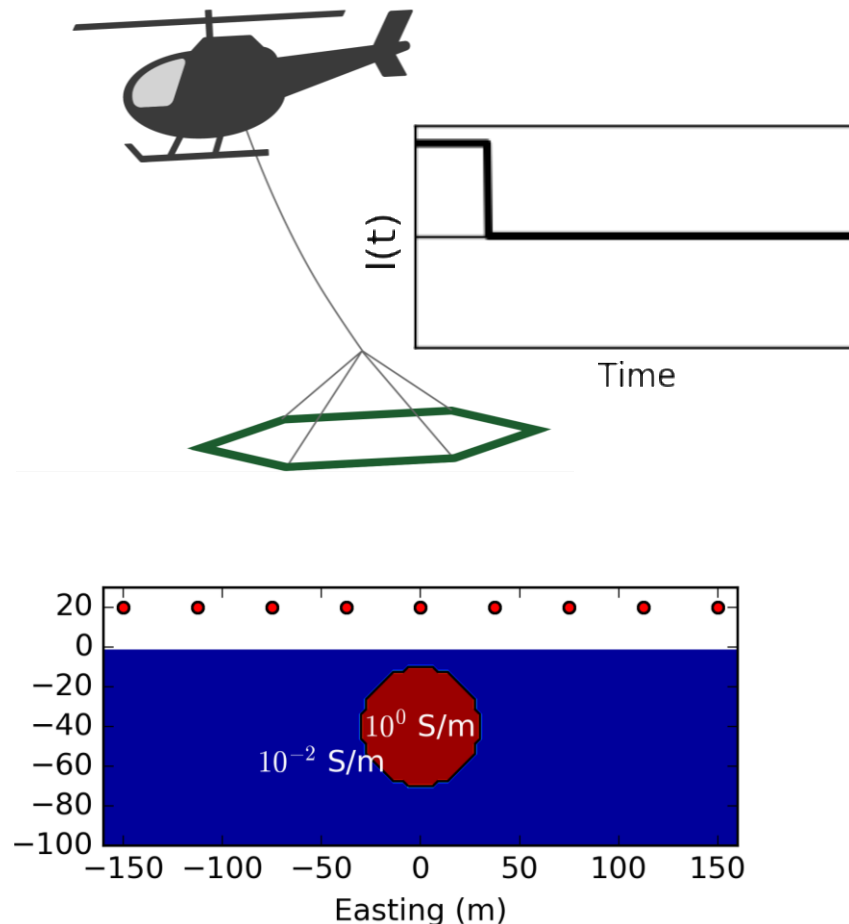


Image credit: Doug Oldenburg, Seogi Kang and Linsey Heagy from UBC-GIF